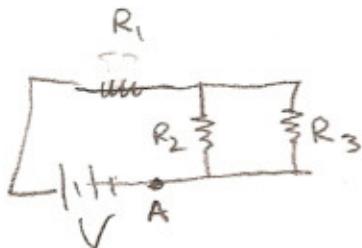


15.



$$R_1 = 5.3\Omega$$

$$R_2 = 10\Omega$$

$$R_3 = 20\Omega$$

$$V = 6 \text{ Volts}$$

$$V = iR \quad (i = ? \text{ battery?})$$

①

$$\frac{1}{R_2} + \frac{1}{R_3} \Rightarrow \boxed{\text{R}_{\text{eff}}}$$

$$\frac{1}{R_{\text{eff}}} = \frac{1}{10\Omega} + \frac{1}{20\Omega}$$

②

$$R_1 \parallel \text{R}_{\text{eff}} \Rightarrow \boxed{\text{R}_T}$$

$$\frac{1}{R_{\text{eff}}} = \frac{30\Omega}{200\Omega^2}$$

$$R_{\text{eff}} = \frac{20}{3}\Omega$$

$$R_T = 5.3\Omega + \frac{20}{3}\Omega = \frac{36}{3}\Omega = 12\Omega$$

③ then

$$\begin{array}{c} R_1 = 12\Omega \\ \text{---} \\ \text{I} \quad V = 6V \end{array} \Rightarrow I = \frac{6V}{12\Omega} = \underline{0.5A}$$

16. Start point A and go around circle (clockwise):

$$+V_{\text{battery}} - V_{R_1} - V_{R_2} = 0$$

$$V_{R_2} = ?$$

$$6V - I_1 R_1 - V_{R_2} = 0$$

but  $I_1 = 0.5A$  from ⑤

so  $6V - (\frac{1}{2}A)(5.3\Omega) - V_{R_2} = 0$

$V_{R_2} = 3.35V$