

PHY 2005 Applied Physics 2 - Summer 2011
Solutions for Suggested Homework Problems (Chapter 20)

2. The definition of capacitance ($C = Q/\Delta V$) yields $Q = C\Delta V = 2.64 \times 10^{-6} \text{ C}$.
6. The capacitance of a parallel plate capacitor is given by $C = \epsilon_0 A/d$. We solve it for the area of the plate to obtain $A = Cd/\epsilon_0 = 102 \text{ m}^2$.
8. We approximate a spherical capacitor with a parallel-plate capacitor of plate area $A = 4\pi r^2 = 0.126 \text{ m}^2$. The capacitance is $C = \epsilon_0 A/d = 2.22 \times 10^{-9} \text{ F}$.
11. (a) If capacitors are connected in series, the reciprocal of the equivalent capacitance is the sum of the reciprocals of the individual capacitances. Therefore, we get $1/C_{eq} = 1/2 + 1/7 + 1/14 = 10/14 \Rightarrow C_{eq} = 1.4 \text{ }\mu\text{F}$. (b) If capacitors are connected in parallel, the equivalent capacitance is the sum of the individual capacitances. We have $C_{eq} = 2+7+14 = 23 \text{ }\mu\text{F}$.
13. (a) When multiple capacitors are connected in parallel across a battery, the potential drop across each capacitor is the same as the potential difference provided by the battery. We obtain $Q_1 = C_1\Delta V = 24 \text{ C}$, $Q_2 = C_2\Delta V = 72 \text{ C}$ and $Q_3 = C_3\Delta V = 144 \text{ C}$ (b) The equivalent capacitance is $1/C_{eq} = 1/2 + 1/6 + 1/12 = 3/4 \Rightarrow C_{eq} = 1.33 \text{ }\mu\text{F}$. Since the capacitors are connected in series, the charge stored in each capacitor is the same as that stored in the equivalent capacitor. $Q_1 = Q_2 = Q_3 = C_{eq}\Delta V = 16 \text{ C}$
14. Electric field between a parallel plate capacitor is constant and is given by $E = \Delta V/d$. (a) $E = 1.14 \times 10^4 \text{ V/m}$ (b) $E = 8.00 \times 10^3 \text{ V/m}$
16. We use the same equation used in the previous problem to get $\Delta V = Ed = 9 \times 10^3 \text{ V}$.
20. The electric field between the two plates is $E = \Delta V/d = 300 \text{ V/m}$. The field exerts Coulomb force of magnitude $F = eE$ on the electron. The force is directed toward the negative plate. Newton's 2nd law yields the acceleration of the electron: $ma = eE \Rightarrow a = eE/m = 5.27 \times 10^{13} \text{ m/s}^2$. The time interval for the electron to pass the region between the two plates of length L is $t = L/v = 8.75 \times 10^{-9} \text{ s}$. During this time interval, the electron is deflected a distance $h = (1/2)at^2 = 2.02 \times 10^{-3} \text{ m}$
23. Electric current is defined as the amount of charge that passes through a cross section of a wire in one second. Therefore, the amount of charge flowing through the bulb in one second is $Q = 0.5 \text{ C}$. Each electron has a charge of magnitude e . The number of electrons is $Q/e = 3.13 \times 10^{18}$.
31. (a) If resistors are connected in series, the equivalent resistance is the sum of the resistances of the individual resistors. $R_{eq} = 2 + 6 + 12 = 20 \text{ }\Omega$. (b) If resistors are connected in parallel, the reciprocal of the equivalent resistance is equal to the sum of the reciprocals of the individual resistances. $1/R_{eq} = 1/2 + 1/6 + 1/12 = 3/4 \Rightarrow R_{eq} = 1.33 \text{ }\Omega$.
35. $R_1 = 5 \text{ }\Omega$ and $R_2 = 4 \text{ }\Omega$ are connected in parallel. The equivalent resistance of these two resistors is $R_{12} = (1/R_1 + 1/R_2)^{-1} = 2.22 \text{ }\Omega$. R_{12} and $R_3 = 3 \text{ }\Omega$ are connected in series. Thus the equivalent resistance of all the three resistors is $R_{eq} = R_{12} + R_3 = 5.22 \text{ }\Omega$.
37. Let $R_1 = 3 \text{ }\Omega$, $R_2 = 10 \text{ }\Omega$, $R_3 = 6 \text{ }\Omega$, $R_4 = 2 \text{ }\Omega$ and $R_5 = 5 \text{ }\Omega$. R_4 and R_5 are connected in series. The equivalent resistance is $R_{45} = R_4 + R_5 = 7 \text{ }\Omega$. R_{45} is connected in parallel with R_3 . We obtain $R_{345} = (1/R_3 + 1/R_{45})^{-1} = 3.23 \text{ }\Omega$. R_1 and R_{345} are connected in series. $R_{1345} = R_1 + R_{345} = 6.23 \text{ }\Omega$. Finally, R_{1345} and R_2 are connected in parallel. Thus the equivalent resistance between a and b is $R_{eq} = (1/R_2 + 1/R_{1345})^{-1} = 3.84 \text{ }\Omega$.
41. Since R_{1345} and R_2 are connected in parallel, the potential drops across them are the same;

they are also the same as the potential difference provided by the battery. The current through the $10\text{-}\Omega$ resistor ($= R_2$) is $I_2 = \Delta V / R_2 = 2\text{ A}$. To find out the current through the $2\text{-}\Omega$ ($= R_4$) resistor, we first calculate the current through R_{1345} . $I_{1345} = \Delta V / R_{1345} = 3.21\text{ A}$. This current flows through resistor R_{345} . Thus the voltage across R_{345} is $\Delta V_{345} = I_{1345} R_{345} = 10.4\text{ V}$. This voltage is the same as that across R_{45} . Therefore, the current flows in resistor R_{45} is $I_{45} = \Delta V / R_{1345} = 1.49\text{ A}$. Since R_4 and R_5 are connected in series, the current through the $2\text{-}\Omega$ resistor is the same as that through R_{45} . The current through the $2\text{-}\Omega$ resistor is 1.49 A .

48. The relation between joule and horsepower is given by $1\text{ hp} = 746\text{ W}$. Therefore, $1/3\text{ hp} = 1/3\text{ hp} \times 746\text{ W} / 1\text{ hp} = 249\text{ W}$. Solving the equation of the power consumption in a circuit ($P = I\Delta V$) for the current to obtain $I = P/\Delta V = 1.91\text{ A}$.

49. (a) We assume all the energy consumed by the heater is used to heat coffee water. Since 1 cal corresponds to 4.186 J , the energy consumed by the heater in 1 minute ($= 60\text{ s}$) is $\Delta E = 10\,000\text{ cal} = 10\,000\text{ cal} \times 4.186\text{ J}/1\text{ cal} = 41\,860\text{ J}$. The definition of power yields $P = \Delta E/\Delta t = 697\text{ W}$. (b) The power consumption equation gives $I = P/\Delta V = 5.80\text{ A}$. (c) We use the definition of resistance to obtain $R = \Delta V/I = 20.7\text{ }\Omega$.

51. The resistance of a wire is related to the resistivity of its material as $R = \rho L/A$. Solving this equation for resistivity, we get $\rho = \pi(D/2)^2 R/L = 1.12 \times 10^{-6}\text{ }\Omega\cdot\text{m}$, where D is the diameter of the wire in meter and R/L is the resistance of the wire per unit meter.

55. The capacitance of the parallel-plate capacitor is $C = Q/\Delta V = 7.5 \times 10^{-10}\text{ F}$. When a dielectric is inserted in a parallel-plate capacitor, its capacitance is given by $C = \kappa\epsilon_0 A/d$. We solve this equation for the separation distance to obtain $d = \kappa\epsilon_0 A/C = \kappa\epsilon_0/C = 8.50 \times 10^{-5}\text{ m}$.