

**PHY 2005 Applied Physics 2 - Summer 2011**  
**Solutions for Suggested Homework Problems (Chapter 21)**

---


1. (a) Kirchhoff's loop rule yields  $6 + 9 - 45I = 0 \Rightarrow I = 0.333 \text{ A}$ . (b) Again we apply the loop rule, we get  $9 - 6 - 45I = 0 \Rightarrow I = 0.0667 \text{ A}$ . Note that the potential drops if you across a battery from its positive to negative terminal.

3. (a)  $I_2$  is flowing into junction A, whereas  $I_1$  and  $I_3$  are flowing out. The junction rule gives  $I_2 = I_1 + I_3$ . (b) We the loop rule to obtain  $+7I_2 + 12 + 5I_1 + 3I_1 - 6 = 0$  Note if you traverse a register in the opposite direction to that of the current flowing through it, the potential rises across the resistor.

7. Two resistors are connected in parallel. The equivalent resistance is  $R_{eq} = (1/15 + 1/6)^{-1} = 4.29 \Omega$ . The current through the battery is  $I_3 = 12 / R_{eq} = 2.8 \text{ A}$ . The voltage across each resistor is the same as the voltage provided by the battery, we get  $I_1 = 12 / R_{eq} = 0.80 \text{ A}$  &  $I_2 = 12 / R_2 = 2.0 \text{ A}$ .

10. The current through the  $6\text{-}\Omega$  resistor is  $0.8/6 = 0.133 \text{ A}$ . Applying the loop rule to loop ABDA, we get  $-6I_1 + 8I_3 + 2 = 0 \Rightarrow I_3 = (6I_1 - 2)/8 = -0.150 \text{ A}$ . The junction rule at point D yields  $0 = I_1 + I_2 + I_3 \Rightarrow I_2 = -I_1 - I_3 = +0.0167 \text{ A}$ . We apply the loop rule to loop CBDC to obtain  $E + 8I_3 = 0 \Rightarrow E = -8I_3 = 1.20 \text{ V}$

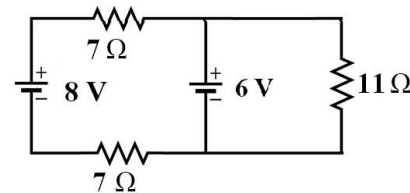14. The three  $2\text{-}\Omega$  resistors are connected in series. The equivalent resistance is  $R = 2 + 2 + 2 = 6 \Omega$ . This equivalent resistor  $R$  is connected in parallel with the  $3\text{-}\Omega$  resistor. The equivalent resistance is  $R' = (1/6 + 1/3)^{-1} = 2 \Omega$ , which is connected in series with  $4\text{-}\Omega$  and  $5\text{-}\Omega$  resistors. We combine the three resistors to obtain  $R'' = 2 + 4 + 5 = 11 \Omega$ . Now we have the circuit shown on the right. The junction rule yields  $I_3 = I_1 + I_2$ . We apply the loop rule to the left loop and the right loop to obtain  $+8 - 7I_1 - 6 - 7I_1 = 0$  &  $6 - 11I_3 = 0$ . Solving the three equation, we get  $I_1 = 0.143 \text{ A}$ ,  $I_2 = 0.402 \text{ A}$  &  $I_3 = 0.545 \text{ A}$



19. All the bulbs are connected in parallel, thus the voltage across each bulb is the same as the provided voltage  $110 \text{ V}$ . (a) Power is given by  $P = I\Delta V$ . This yields  $I = 60/110 = 0.545 \text{ A}$ . (b) The current through the right switch is the sum of the current through the  $100\text{-W}$  bulb and  $40\text{-W}$  bulb.  $I = 100/110 + 40/110 = 1.27 \text{ A}$ . (c) The current through the fuse is equal to the sum of the current through individual bulbs.  $I = \Sigma(P/\Delta V) = (1/\Delta V)\Sigma P = (60 + 100 + 100 + 40)/110 = 2.73 \text{ A}$ .

23. While a battery is discharging, the terminal potential difference of the battery is  $\Delta V = E - rI = 1.39 \text{ V}$  (b) For charging, the terminal p.d. is given by  $\Delta V = E + rI = 1.75 \text{ V}$ .

24. The loop rule yields the terminal voltage of the cell:  $\Delta V - RI = 0 \Rightarrow \Delta V = RI = 0.36 \text{ V}$ . The terminal voltage is smaller than the emf due to potential drop across the internal resistor. The internal resistance is  $\Delta V = E - rI \Rightarrow r = (E - \Delta V)/I = 9.92 \Omega$

26. The ampere-hour is a unit of charge. The total charge carried by a current is  $Q = I\Delta t$ . We solve this for the time to obtain  $\Delta t = Q/I = 26.7 \text{ h}$ . (b) The total energy stored in a battery is  $E = P\Delta t = I\Delta V\Delta t = 3.46 \times 10^6 \text{ J}$ . Note that you have to express the time interval  $\Delta t$  in seconds.

28. (a) The definition of resistance yields  $I = \Delta V/R = 5.03 \times 10^{-4} \text{ A}$ . (b) The voltage across the resistor is the same as the terminal voltage of the battery. We solve  $\Delta V = E - rI$  for  $r$  to get  $r = (E - \Delta V)/I = 91.4 \Omega$ .

33. The number of silver atoms plated out by electroplating is the same as the number of electrons flowing through the circuit. Thus the mass of the plated out silver is  $m = nm_{atom} = (I\Delta t/e)m_{atom}$ . Solving this equation, we obtain  $m_{atom} = (me/I\Delta t) = 1.75 \times 10^{-25} \text{ kg}$

36. Let  $I_2$  be the current flowing through the switch  $K$ . Applying Kirchhoff's loop rule to the largest loop, we get  $6 - 6I_2 - 4I_2 = 0 \Rightarrow I_2 = 0.60 \text{ A}$ . The loop rule applied to the loop through the two batteries yields  $6 - 2I_1 - 6 - 3I_1 = 0 \Rightarrow I_1 = 0$ . We apply the loop rule to the left triangular loop to obtain  $+2I_1 - 6I_2 + \Delta V_C = 0 \Rightarrow \Delta V_C = 3.6 \text{ V}$ . The charge on the capacitor is  $Q = C\Delta V_C = 7.2 \times 10^{-6} \text{ C}$ .

37. Apply the loop rule to the left triangular loop, we obtain  $xI_2 + R_1I_1 = 0 \Rightarrow I_1/I_2 = x/R_1$ . The loop rule applied to the right triangular loop yields  $R_2I_2 - R_3I_1 = 0 \Rightarrow I_1/I_2 = R_2/R_3$ . Equating these two equations, we get  $x/R_1 = R_2/R_3 \Rightarrow x = R_1(R_2/R_3)$

39.  $R_3$  and  $R_4$  are connected in series, they have the equivalent resistance of  $R_{34} = 4 + 2 = 6 \Omega$ . The loop rule applied to the top loop yields  $3 - 7I_1 + 3I_2 - 2 = 0$ . Applying the loop rule to the bottom loop, we obtain  $2 - 3I_2 + 6I_3 - 4 = 0$ . The junction rule yields  $I_1 + I_2 + I_3 = 0$ . Solving the three equations simultaneously for  $I_3$ , we obtain  $I_3 = 0.210 \text{ A}$

44. Kirchhoff's loop rule yields  $3 - 2I - 2I - 1I - 2 - 6I = 0 \Rightarrow I = 0.0909 \text{ A}$ . The power consumed in  $R_1$  is  $P = I^2R_1 = 0.0165 \text{ W}$ . This is the heat generated in  $R_1$ . Thus the time it takes to generate  $18 \text{ J}$  of heat is  $\Delta t = W/P = 1090 \text{ s} = 18.18 \text{ min}$

47. The current flowing in the circuit is  $I = \sqrt{P/R} = \pm 1.83 \text{ A}$ . The loop rule yields  $E_1 - 1I - 3I - 4I - 2I - 28 = 0$ . Plugging the values of  $I$ , we obtain  $E_1 = 46.2 \text{ V}, 9.7 \text{ V}$