
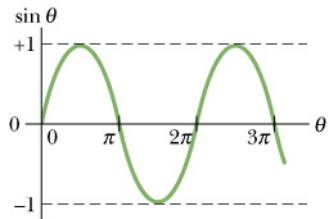





Chapter 31: RLC Circuits

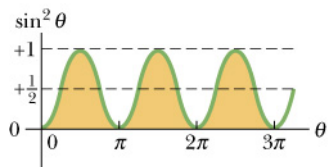

(a)



(b)

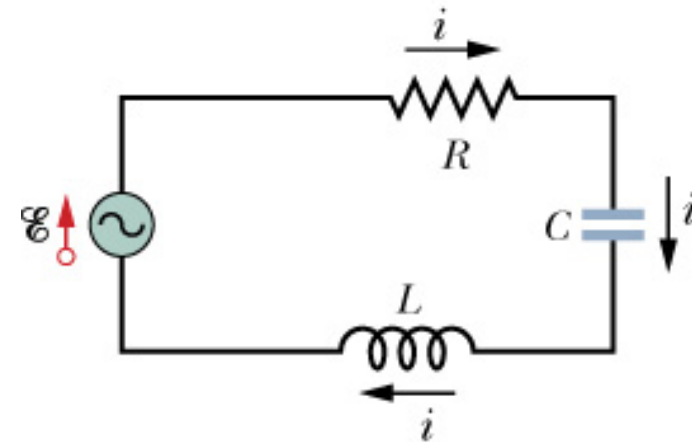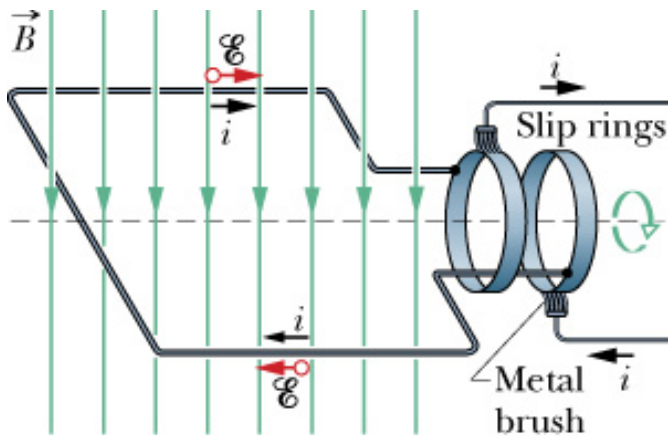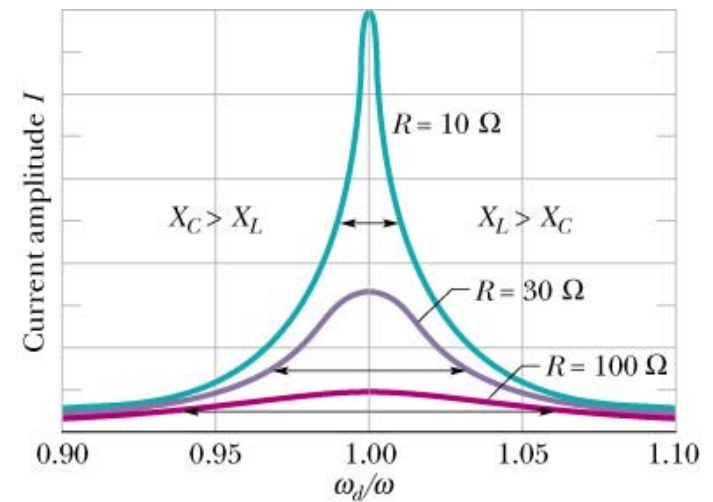

Topics

→ LC Oscillations

- ◆ Conservation of energy

→ Damped oscillations in RLC circuits

- ◆ Energy loss

→ AC current


- ◆ RMS quantities

→ Forced oscillations

- ◆ Resistance, reactance, impedance
- ◆ Phase shift
- ◆ Resonant frequency
- ◆ Power

→ Transformers


- ◆ Impedance matching

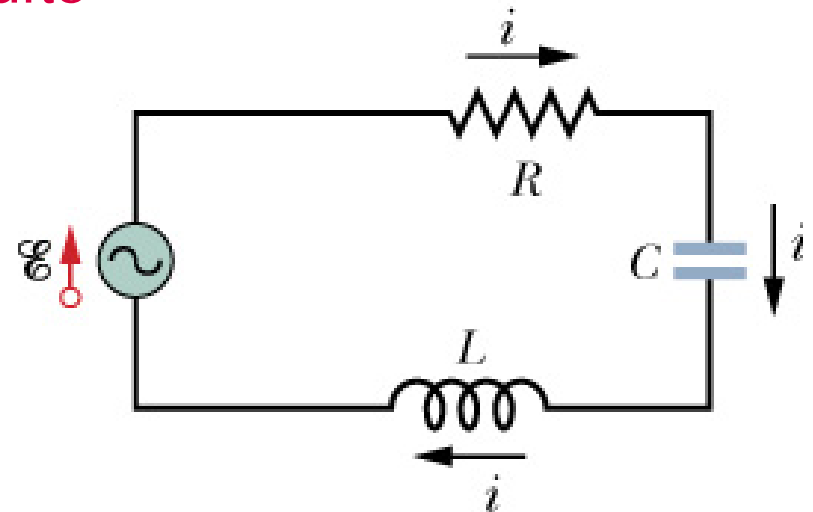

LC Oscillations

→ Work out equation for LC circuit (loop rule)

$$-\frac{q}{C} - L \frac{di}{dt} = 0$$

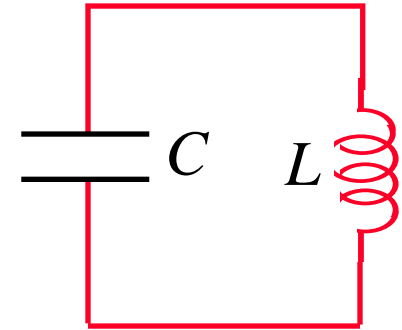

→ Rewrite using $i = dq/dt$

$$L \frac{d^2q}{dt^2} + \frac{q}{C} = 0 \Rightarrow \frac{d^2q}{dt^2} + \omega^2 q = 0$$

$$\omega = \frac{1}{\sqrt{LC}}$$

◆ ω (angular frequency) has dimensions of 1/t

→ Identical to equation of mass on spring

$$m \frac{d^2x}{dt^2} + kx = 0 \Rightarrow \frac{d^2x}{dt^2} + \omega^2 x = 0$$

$$\omega = \sqrt{\frac{k}{m}}$$



LC Oscillations (2)

→ Solution is same as mass on spring \Rightarrow oscillations

$$q = q_{\max} \cos(\omega t + \theta) \quad \omega = \sqrt{\frac{k}{m}}$$

- ◆ q_{\max} is the maximum charge on capacitor
- ◆ θ is an unknown phase (depends on initial conditions)


→ Calculate current: $i = dq/dt$

$$i = -\omega q_{\max} \sin(\omega t + \theta) = -i_{\max} \sin(\omega t + \theta)$$

→ Thus both charge and current oscillate

- ◆ Angular frequency ω , frequency $f = \omega/2\pi$
- ◆ Period: $T = 2\pi/\omega$
- ◆ Current and charge differ in phase by 90°

Plot Charge and Current vs t

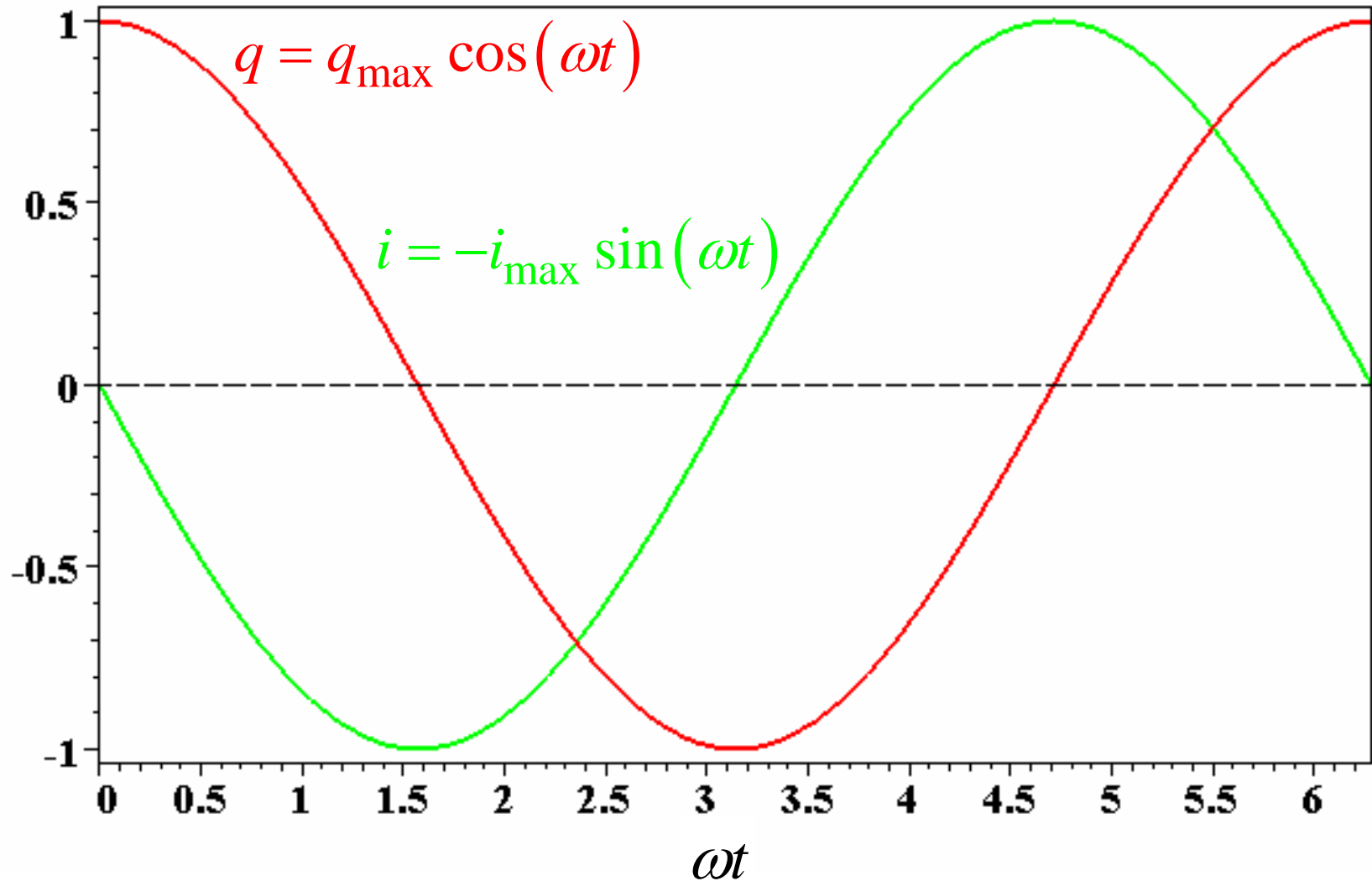

Energy Oscillations in LC Circuits

→ Total energy in circuit is conserved. Let's see why

$$L \frac{di}{dt} + \frac{q}{C} = 0$$

Equation of LC circuit

$$L \frac{di}{dt} i + \frac{q}{C} \frac{dq}{dt} = 0$$

Multiply by $i = dq/dt$

$$\frac{L}{2} \frac{d}{dt} (i^2) + \frac{1}{2C} \frac{d}{dt} (q^2) = 0$$

Use $\frac{dx^2}{dt} = 2x \frac{dx}{dt}$

$$\frac{d}{dt} \left(\frac{1}{2} Li^2 + \frac{1}{2} \frac{q^2}{C} \right) = 0$$

$$\frac{1}{2} Li^2 + \frac{1}{2} \frac{q^2}{C} = \text{const}$$

$$U_L + U_C = \text{const}$$

Oscillation of Energies

→ Energies can be written as (using $\omega^2 = 1/LC$)

$$U_C = \frac{q^2}{2C} = \frac{q_{\max}^2}{2C} \cos^2(\omega t + \theta)$$


$$U_L = \frac{1}{2} Li^2 = \frac{1}{2} L\omega^2 q_{\max}^2 \sin^2(\omega t + \theta) = \frac{q_{\max}^2}{2C} \sin^2(\omega t + \theta)$$

→ Conservation of energy: $U_C + U_L = \frac{q_{\max}^2}{2C} = \text{const}$

→ Energy oscillates between capacitor and inductor

- ◆ Endless oscillation between electrical and magnetic energy
- ◆ Just like oscillation between potential energy and kinetic energy for mass on spring

Plot Energies vs t

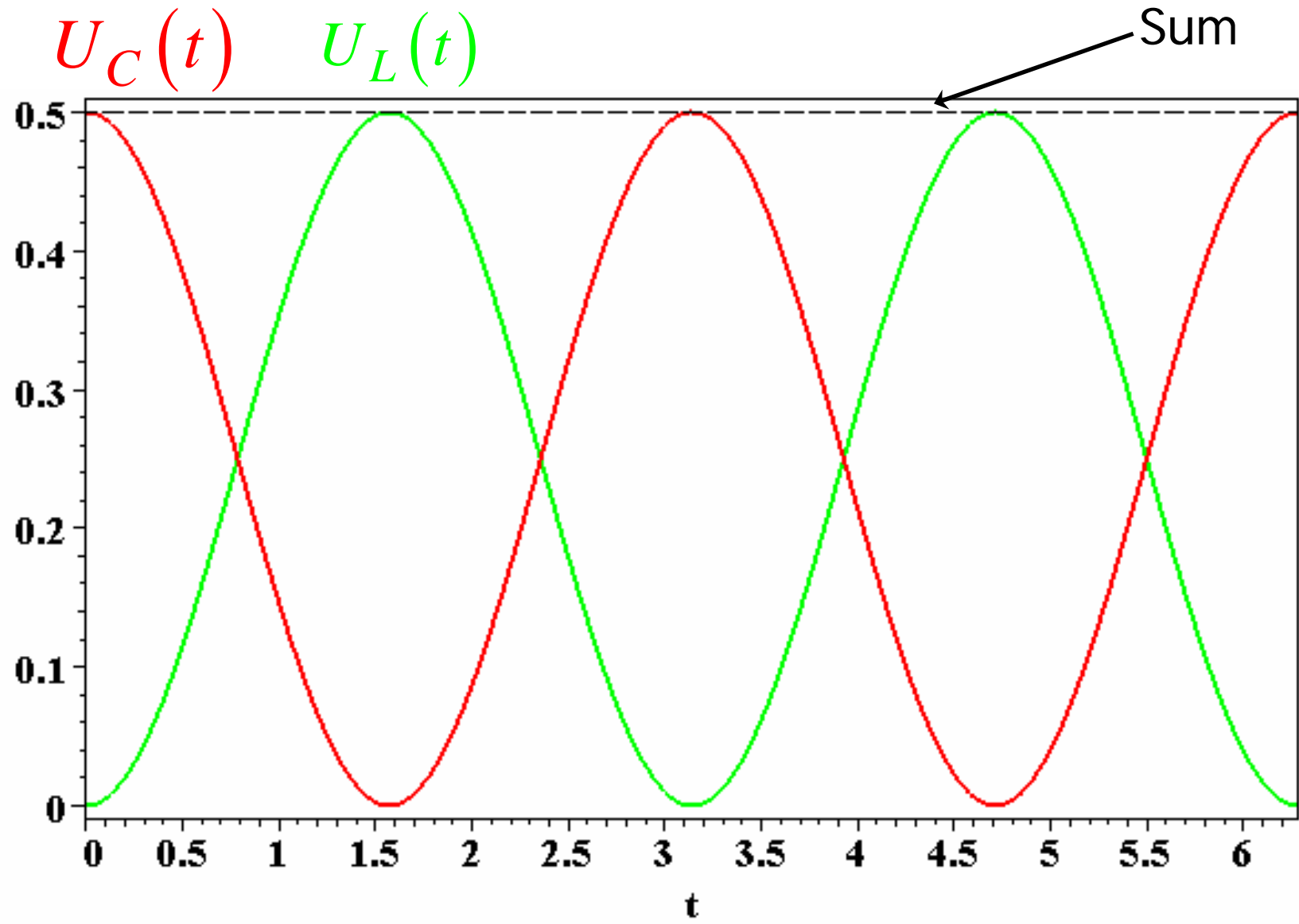

LC Circuit Example

→Parameters

- ◆ $C = 20\mu\text{F}$
- ◆ $L = 200\text{ mH}$
- ◆ Capacitor initially charged to 40V, no current initially

→Calculate ω , f and T

- ◆ $\omega = 500\text{ rad/s}$ $\omega = 1/\sqrt{LC} = 1/\sqrt{(2 \times 10^{-5})(0.2)} = 500$
- ◆ $f = \omega/2\pi = 79.6\text{ Hz}$
- ◆ $T = 1/f = 0.0126\text{ sec}$

→Calculate q_{max} and i_{max}

- ◆ $q_{\text{max}} = CV = 800\ \mu\text{C} = 8 \times 10^{-4}\text{ C}$
- ◆ $i_{\text{max}} = \omega q_{\text{max}} = 500 \times 8 \times 10^{-4} = 0.4\text{ A}$

→Calculate maximum energies

- ◆ $U_C = q_{\text{max}}^2/2C = 0.016\text{J}$ $U_L = Li_{\text{max}}^2/2 = 0.016\text{J}$

LC Circuit Example (2)

→ Charge and current

$$q = 0.0008 \cos(500t) \quad i = \frac{dq}{dt} = -0.4 \sin(500t)$$

→ Energies

$$U_C = 0.016 \cos^2(500t) \quad U_L = 0.016 \sin^2(500t)$$

→ Voltages

$$V_C = q / C = 40 \cos(500t)$$

$$V_L = L di / dt = -L\omega i_{\max} \cos(500t) = -40 \cos(500t)$$

→ Note how voltages sum to zero, as they must!


Quiz

→ Below are shown 3 LC circuits. Which one takes the least time to fully discharge the capacitors during the oscillations?


◆ (1) A

◆ (2) B


◆ (3) C

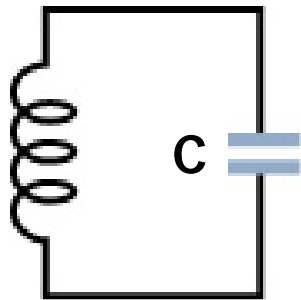

A

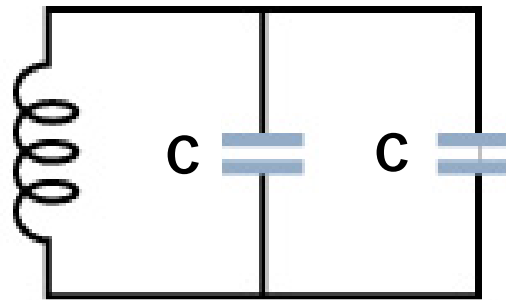

B

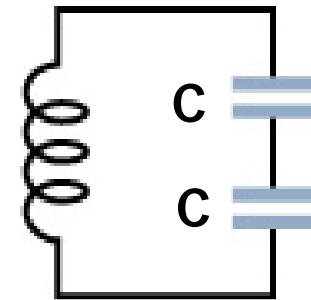

C

$$\omega = 1/\sqrt{LC}$$

C has smallest capacitance, therefore highest frequency, therefore shortest period

RLC Circuit

→ The loop rule tells us

$$L \frac{di}{dt} + Ri + \frac{q}{C} = 0$$

→ Use $i = dq/dt$, divide by L


$$\frac{d^2q}{dt^2} + \frac{R}{L} \frac{dq}{dt} + \frac{q}{LC} = 0$$

→ Solution slightly more complicated than LC case


$$q = q_{\max} e^{-tR/2L} \cos(\omega' t + \theta) \quad \omega' = \sqrt{1/LC - (R/2L)^2}$$

→ This is a damped oscillator (similar to mechanical case)

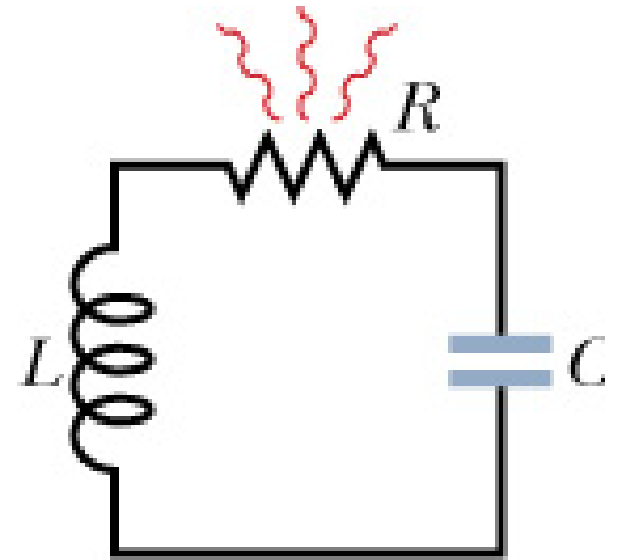◆ Amplitude of oscillations falls exponentially



Charge and Current vs t in RLC Circuit

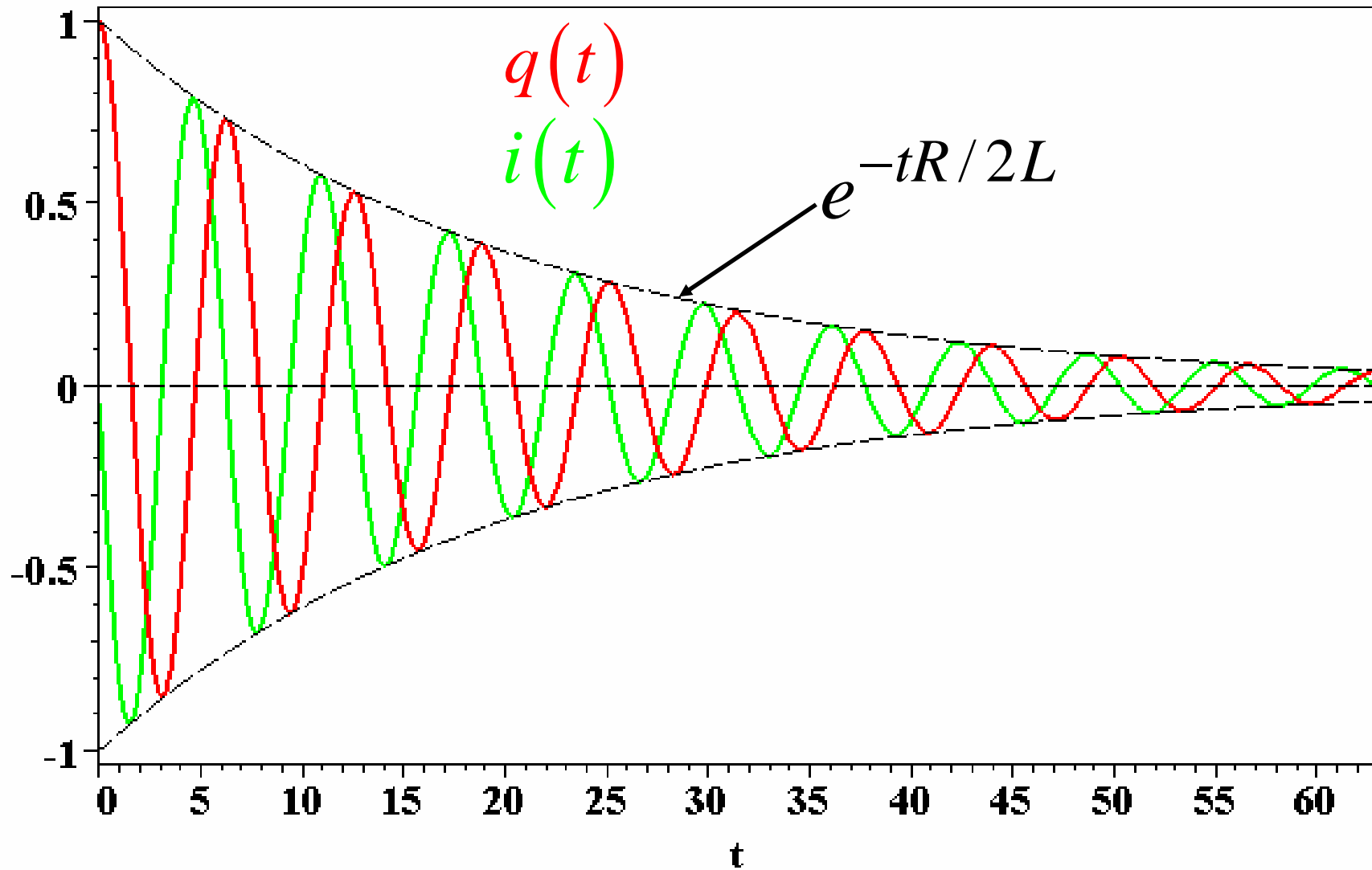

RLC Circuit Example

→ Circuit parameters

◆ $L = 12\text{mL}$, $C = 1.6\mu\text{F}$, $R = 1.5\Omega$

→ Calculate ω , ω' , f and T

◆ $\omega = 7220 \text{ rad/s}$

$$\omega = 1/\sqrt{(0.012)(1.6 \times 10^{-6})} = 7220$$

◆ $\omega' = 7220 \text{ rad/s}$

$$\omega' = \sqrt{7220^2 - (1.5/0.024)^2} \approx \omega$$

◆ $f = \omega/2\pi = 1150 \text{ Hz}$

◆ $T = 1/f = 0.00087 \text{ sec}$

→ Time for q_{max} to fall to $1/2$ its initial value $e^{-tR/2L} = 1/2$

◆ $t = (2L/R) * \ln 2 = 0.0111\text{s} = 11.1 \text{ ms}$

◆ # periods = $0.0111/0.00087 \approx 13$

RLC Circuit (Energy)

$$L \frac{di}{dt} + Ri + \frac{q}{C} = 0$$

Basic RLC equation

$$L \frac{di}{dt} i + Ri^2 + \frac{q}{C} \frac{dq}{dt} = 0$$

Multiply by $i = dq/dt$

$$\frac{d}{dt} \left(\frac{1}{2} Li^2 + \frac{1}{2} \frac{q^2}{C} \right) = -i^2 R$$

Collect terms
(similar to LC circuit)

$$\frac{d}{dt} (U_L + U_C) = -i^2 R$$

Total energy in circuit
decreases at rate of $i^2 R$
(dissipation of energy)

$$U_{\text{tot}} \sim e^{-tR/L}$$

Energy in RLC Circuit

