

Exam 3 Solutions

1. (*Prob. 30.60*) A coil with inductance 1.9 H and a 10 Ω resistor are connected in series to an ideal battery of voltage 95 V. At 0.10 sec after the connection is made, what is current in the circuit (in amps)?

- (1) 3.9
- (2) 5.6
- (3) 8.1
- (4) 0
- (5) 1.4

The current in a LR circuit is given by $i = \frac{V}{R}(1 - e^{-tR/L})$. Plugging in values for t , R , L and V gives $I = 3.9$ A.

2. (*F2005 exam*) A tightly-wound circular wire loop of 6 cm radius and 8 turns rotates around its diameter at 55 Hz inside a solenoid of radius 18 cm and 4.2 T B field. If the wire loop has a resistance of 0.067 Ω , what is the rms current induced in the loop in amps?

- (1) 1,390
- (2) 330
- (3) 173
- (4) 12,500
- (5) 560

The induced emf is given by Faraday's law as $\mathcal{E} = -Nd\Phi_B/dt$, where $\Phi_B = \pi r^2 B \cos \omega t$. Taking the derivative, and using $\omega = 2\pi f$, we get $\mathcal{E} = N\pi r^2 2\pi f B \sin 2\pi ft$, so the rms emf is $\mathcal{E}_{\text{rms}} = \sqrt{2}N\pi^2 r^2 f B$, which includes a factor of $1/\sqrt{2}$ to convert from peak to rms. Using the values given, we get $\mathcal{E}_{\text{rms}} = 92.8\text{V}$ and $I_{\text{rms}} = \mathcal{E}_{\text{rms}}/R = 1390$ A.

3. A series RLC circuit is driven by an AC emf source of a fixed frequency. In order to make this circuit more inductive you need to decrease:

- (1) its natural frequency
- (2) its resistance
- (3) its inductance
- (4) its capacitance
- (5) the amplitude of the emf

The natural (angular) frequency is given by $\omega = 1/\sqrt{LC}$. Decreasing it is equivalent to increasing the inductance (increasing inductive reactance) or increasing the capacitance (decreasing capacitive reactance), both of which increase the relative amount of inductive reactance.

4. (**WebAssign 31.56**) A dimmer for a stage light at a theater consists of a variable inductor, whose inductance is adjustable between zero and L_{\max} , connected in series with a lightbulb. The electrical supply is 120 V (rms) at 60.0 Hz; the lightbulb is rated at 1.0 kW for this voltage. What L_{\max} is required if you want the rate of energy dissipation in the lightbulb to be variable by a factor of 10 from its upper limit of 1.0 kW? Assume that the resistance of the lightbulb does not depend on its temperature.

- (1) 0.11 H
- (2) 0.45 H
- (3) 1.2 H
- (4) 65 mH
- (5) 21 mH

The energy dissipation is given by $P = I^2 R = (V/Z)^2 R = V^2 R / (X_L^2 + R^2)$. To get a ratio of 10 to 1, X_L must range from 0 to $3R$. Using $X_L = \omega L$, with $\omega = 120\pi$, we see that $L_{\max} = 0.11$ H.


5. (*Modified sample problem 31.8*) A series RLC circuit consists of a 0.10Ω resistor, a $3.0 \mu\text{H}$ inductor, and a capacitor of an unknown value C . When driven with an AC emf source, the circuit resonates at 100.0 kHz . Find C .

- (1) $0.84 \mu\text{F}$
- (2) $0.16 \mu\text{F}$
- (3) $2.3 \mu\text{F}$
- (4) $9.4 \mu\text{F}$
- (5) No capacitance can cause the circuit to resonate at this frequency.

The natural frequency is given by $f_0 = 1/2\pi\sqrt{LC}$. To make the circuit resonant, we must have the driving frequency $f_d = f_0$. Using $f_d = 10^5$ and the given value of L , we calculate $C = 0.84 \mu\text{F}$.

6. (*Similar to lecture problem*) In the figure shown, a uniform field (call it field 1) is directed into the page within a circular region. As the strength of this field increases with time, another field (field 2) appears in the clockwise direction as a result. Which of the following can be correct?

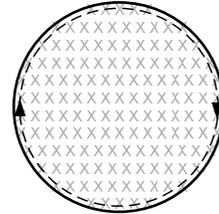- (1) Field 1 is an electric field and field 2 a magnetic field.
- (2) Field 1 is a magnetic field and field 2 an electric field.
- (3) Fields 1 and 2 are both electric fields.
- (4) Fields 1 and 2 are both magnetic fields.
- (5) No field 1 can produce field 2 in the clockwise direction.



The only possible options are (1) or (2). One can see from the directions that (1) is the answer.

7. (*From lecture*) To which of the following did Maxwell add a new term, completing the theory of electricity and magnetism?

- (1) Ampere's law
- (2) Gauss' law
- (3) Coulomb's law
- (4) the Biot-Savart law
- (5) Faraday's law

Maxwell added the displacement current term to Ampere's law, as discussed in lecture.

8. (*Similar to WebAssign and lecture*) A laser beam with intensity 10^6 W/m^2 and wavelength 632.8 nm is aimed vertically upward. What is the maximum radius in nm of a spherical particle of graphite (density 2100 kg/m^3) that can be supported by the laser beam against gravity ($g = 9.8 \text{ m/s}^2$)? Assume that the particle is totally absorbing.

- (1) 120
- (2) 490
- (3) 1190
- (4) 230
- (5) 190

The total force on the particle is $F = I\pi r^2 / c$ and its mass is $m = 4\pi r^3 \rho / 3$. Thus to balance the particle against gravity, we must have $I\pi r^2 / c = 4\pi r^3 \rho g / 3$. Solving for the maximum value of r yields $r = 3I / 4\rho g c$. The values shown yield $r = 120 \text{ nm}$.

9. (*Similar to lecture problem*) A small light bulb is placed 3 cm inside a solid cube of lucite ($n=1.50$) and turned on. What is the radius (in cm) of the illuminated circle that would be seen by an observer standing above the lucite block?

- (1) 2.68
- (2) 3.00
- (3) 3.35
- (4) 4.50
- (5) 3.42

Only the light that hits the water surface at less than the critical angle ($\sin \theta_c = 1/n$) will emerge from the water. The radius of the circle from which light emerges is thus $r = h \tan \theta_c$, where h is the depth of the light bulb. A quick calculation yields $\theta_c = 41.8^\circ$ and $r = 2.68 \text{ cm}$.

10. (*Similar to sample problem 33.3*) A horizontal beam of unpolarized light is incident upon a stack of 4 polarizers with axes of polarization, in order and measured clockwise from the vertical, at 30° , 75° , 120° and 180° . What is the ratio of the intensity of the transmitted beam to that of the incident beam?

- (1) 0.031
- (2) 0.063
- (3) 0.023
- (4) 0.047
- (5) 0.0063

Let I_0 be the initial intensity. The final intensity I is given by the expression, which depends only on relative angles, $I = I_0 \frac{1}{2} \cos^2 45^\circ \cos^2 45^\circ \cos^2 60^\circ = I_0 / 32$. The first factor of $1/2$ comes from unpolarized light going through the first filter.