
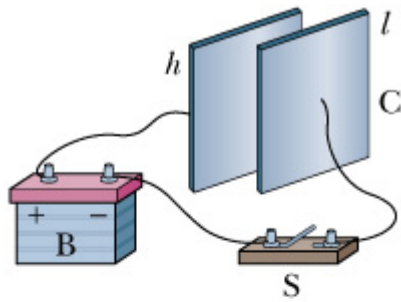



Capacitance

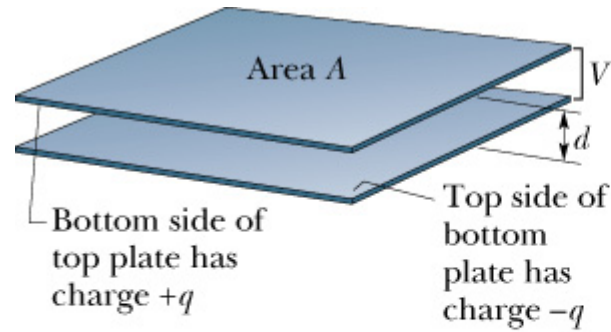


(a)




(a)

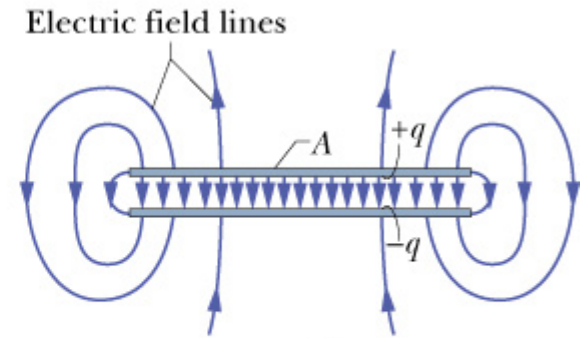


(b)

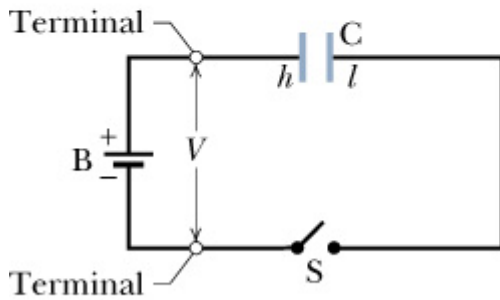


(b)

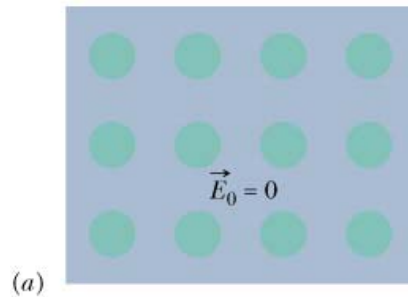

(a)

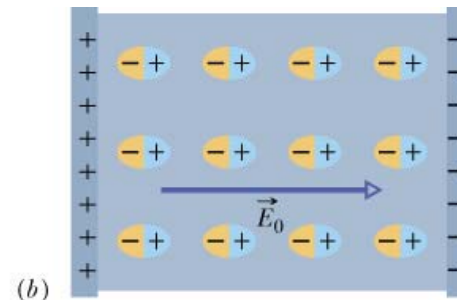

(b)

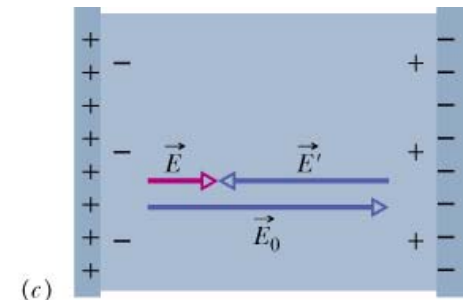

(c)

Purpose of Capacitors

→ Storage of charge: $Q = CV$

◆ Used in DC and AC circuits

→ Storage of energy

◆ Can provide energy to circuits

→ Used in DC and AC circuits

◆ Timing in DC circuits

◆ Resonance in AC circuits

◆ (Later in course)

$$U = \frac{Q^2}{2C} = \frac{1}{2}CV^2$$

Capacitors in Parallel


→ $V_1 = V_2 = V_3$ (same potential top and bottom)

→ Total charge: $q_{\text{tot}} = q_1 + q_2 + q_3$

→ $C_{\text{eq}}V = C_1V + C_2V + C_3V$

$$C_{\text{eq}} = C_1 + C_2 + C_3$$

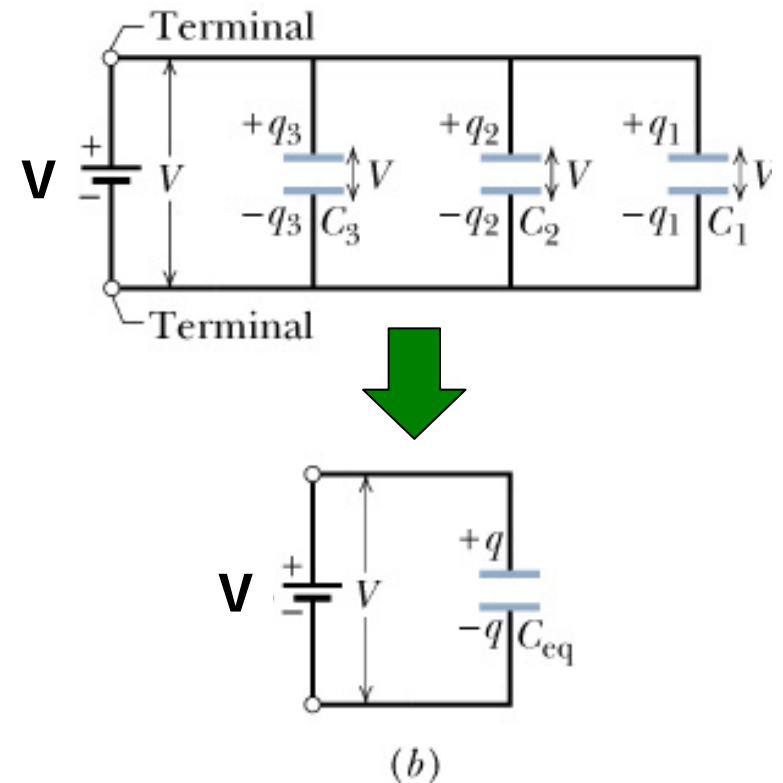- Basic law for combining capacitors in parallel
- Works for N capacitors



Capacitors in Series



→ $q_1 = q_2 = q_3$ (same current charges all capacitors)

→ Total potential: $V = V_1 + V_2 + V_3$

→ $q/C_{eq} = q/C_1 + q/C_2 + q/C_3$

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

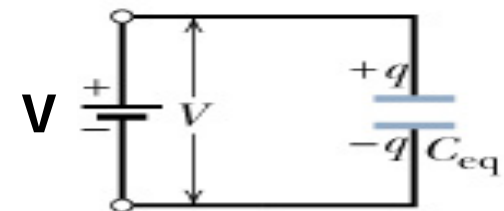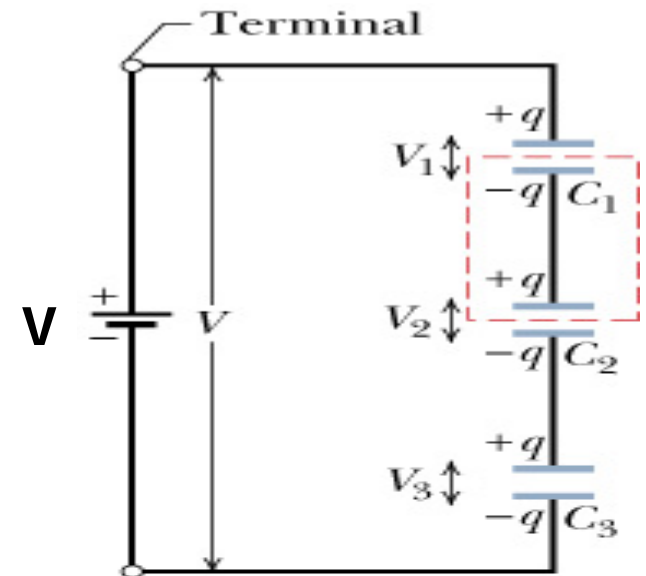- Basic law for combining capacitors in series
- Works for N capacitors



(b)

ConceptTest

→ Two identical parallel plate capacitors are shown in an end-view in Figure A. Each has a capacitance of C .

If the two are joined together at the edges as in Figure B, forming a single capacitor, what is the final capacitance?

◆ (a) $C/2$


◆ (b) C

◆ (c) $2C$

◆ (d) 0

◆ (e) Need more information

Area is doubled

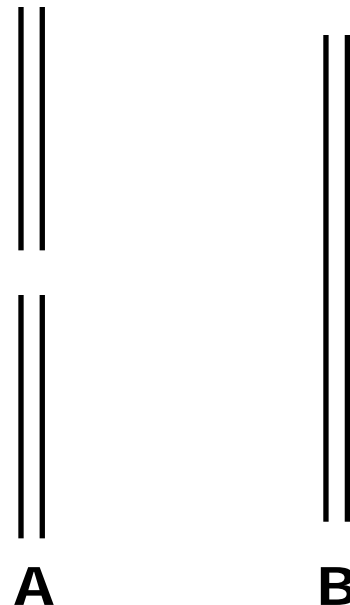

ConceptTest


→ Each capacitor is the same in the three configurations.
Which configuration has the lowest equivalent capacitance?

◆ (1) A


◆ (2) B $C/2$ (series)

◆ (3) C

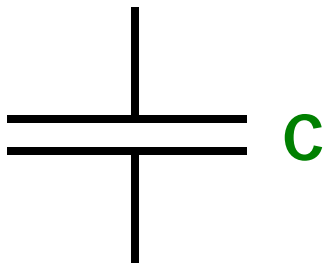
◆ (4) They all have identical capacitance



A

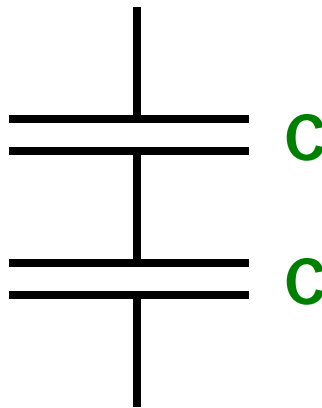

B

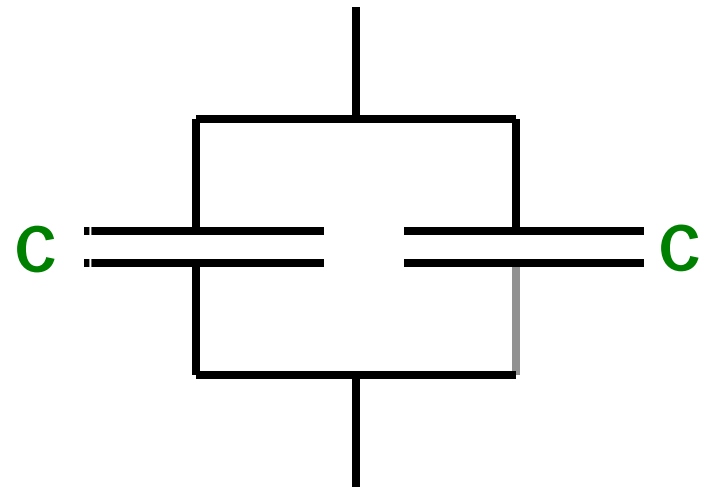

C

Capacitors in Circuits

→ Find total capacitance C_{eq} between (a) and (b)

◆ Use multi-step process


→ $C_{23} = 2 + 3$ in series

◆ $1/C_{23} = 1/C + 1/C = 2/C$

◆ $C_{23} = C/2$

→ $C_1 + C_{23}$ in parallel

◆ $C_{eq} = C + C/2 = 3C/2$

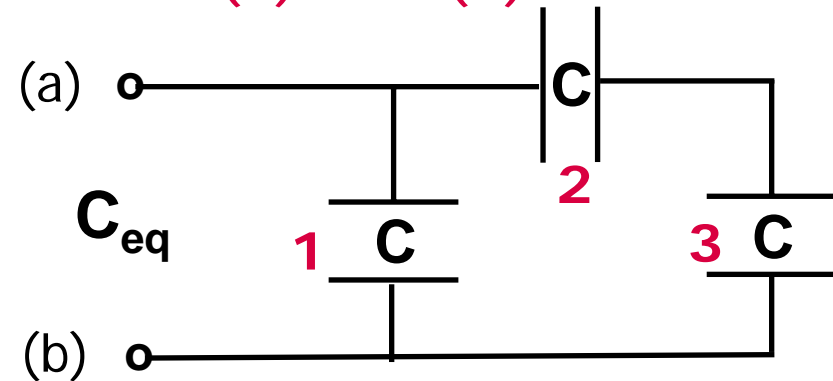

Another Example


→ Assume all capacitors = $10 \mu\text{F}$. Find total capacitance

◆ C_3 and C_4 in parallel: $C_{34} = 10 + 10 = 20 \mu\text{F}$

◆ C_1, C_{34}, C_2 in series

$$\frac{1}{C_{\text{eq}}} = \frac{1}{10} + \frac{1}{20} + \frac{1}{10} = \frac{5}{20}$$

$$C_{\text{eq}} = 4.0 \mu\text{F}$$

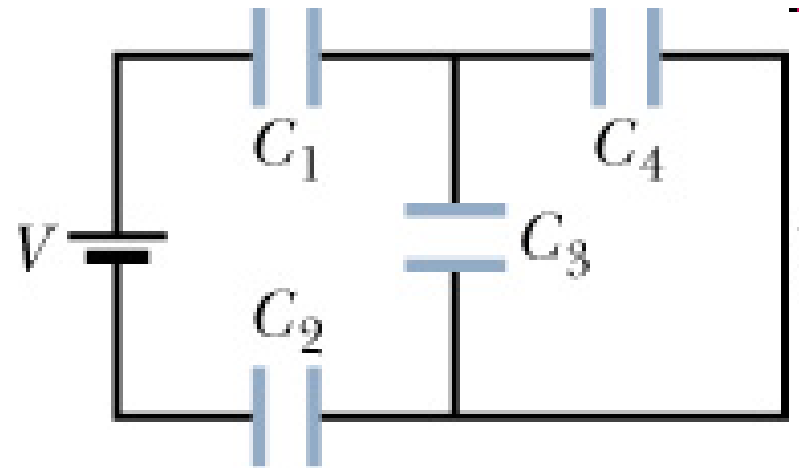

→ How much charge provided by battery to fully charge capacitors? Assume $V = 20$.

◆ $Q = C_{\text{eq}} \times V = 4 \times 20 = 80 \mu\text{C}$


Another Example

→ Assume all capacitors = $10 \mu\text{F}$. Find total capacitance

- ◆ $C_{234} = 30 \mu\text{F}$ (parallel)
- ◆ $C_{56} = 20 \mu\text{F}$ (parallel)
- ◆ C_1, C_{234}, C_{56} (series)

$$\frac{1}{C_{\text{eq}}} = \frac{1}{10} + \frac{1}{30} + \frac{1}{20} = \frac{11}{60}$$


$$C_{\text{eq}} = 5.45 \mu\text{F}$$

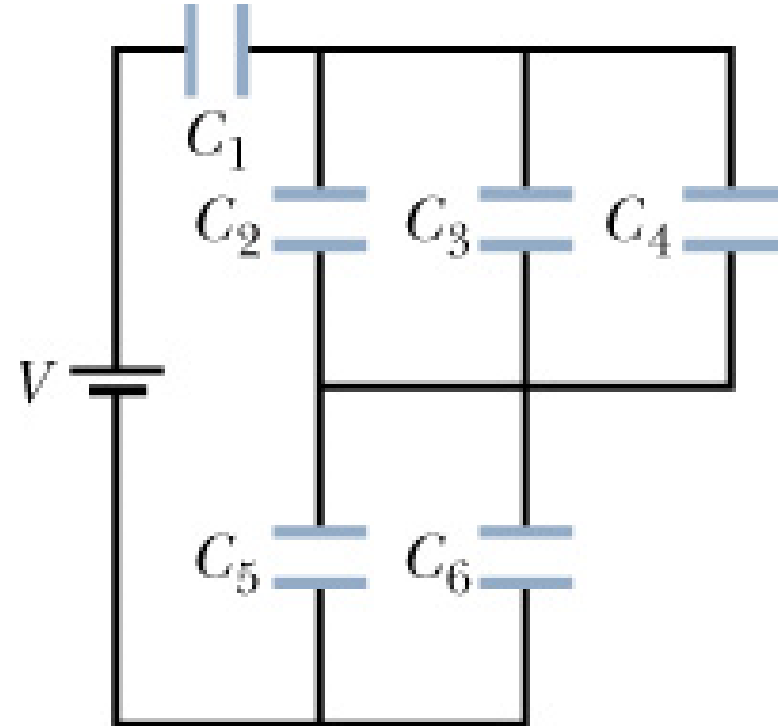

→ How much charge provided by battery to fully charge capacitors? Assume $V = 20$.

- ◆ $Q = C_{\text{eq}} \times V = 5.45 \times 20 = 109 \mu\text{C}$

Find Charges on Series Capacitors

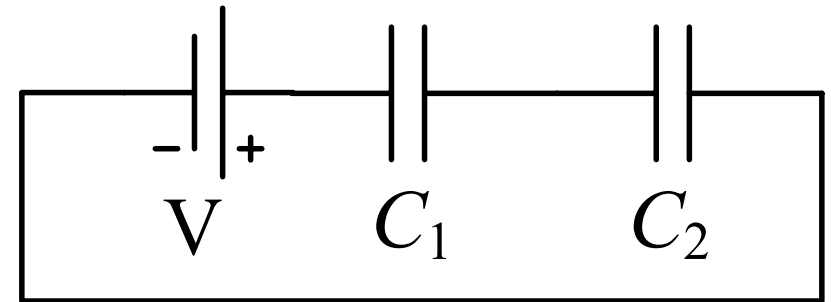

→ Let $V = 10$, $C_1 = 6\mu\text{F}$, $C_2 = 12\mu\text{F}$

◆ Find charges, voltages on C_1 , C_2

→ Combine series capacitances

◆ This is what battery "sees"!

$$C_{\text{eq}} = \frac{C_1 C_2}{C_1 + C_2} = \frac{72}{18} = 4\mu\text{F}$$

→ Find q_{eq} , then use $q_{\text{eq}} = q_1 = q_2$

◆ $q_{\text{eq}} = C_{\text{eq}} V = 4 \times 10 = 40 \mu\text{C}$

→ Find V_1 , V_2

◆ $V_1 = q_1 / C_1 = 40 / 6 = 6.67 \text{ V}$

◆ $V_2 = q_2 / C_2 = 40 / 12 = 3.33 \text{ V}$

◆ $V_1 + V_2 = 10$, as expected

Example: Find q_i and V_i on All Capacitors

→ C_1 is charged in position A, then S is thrown to B position

◆ Initial voltage across C_1 : $V_0 = 12$

◆ Initial charge on C_1 : $q_{10} = 12 \times 4 = 48\mu\text{C}$

→ After switch is thrown to B:

◆ Charge flows from C_1 to C_2 and C_3

◆ $V_1 = V_{23}$ (parallel branches)

→ q_2 and q_3 in series: $q_2 = q_3 = q_{23}$ ($C_{23} = 2\mu\text{F}$)

◆ Charge conservation: $q_{10} = q_1 + q_{23}$

◆ $48 = C_1 V_1 + C_{23} V_1$ ($V_1 = V_{23}$)


◆ Find V_1 : $V_1 = 48 / (C_1 + C_{23}) = 8 \text{ V}$

◆ Find q_1 : $q_1 = C_1 V_1 = 32\mu\text{C}$

◆ $q_{23} = 48 - 32 = q_2 = q_3 = 16\mu\text{C}$

◆ $V_2 = q_2 / C_2 = 2.67 \text{ V}$

◆ $V_3 = q_3 / C_3 = 5.33 \text{ V}$

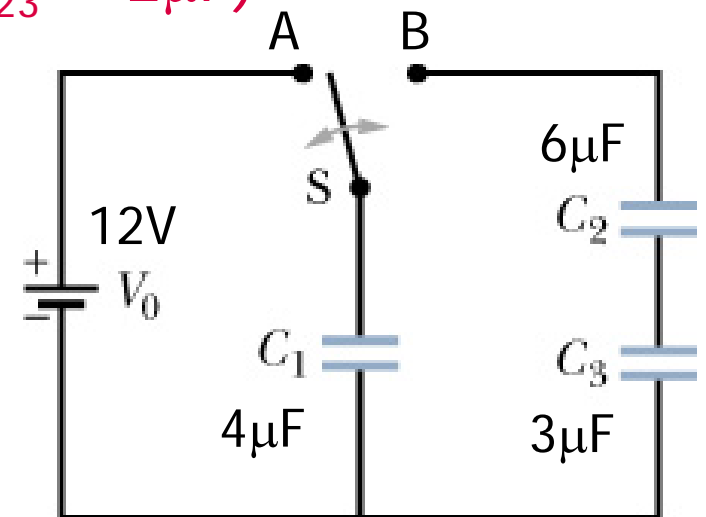

Another Example

→ Each capacitor has $C = 10\mu\text{F}$. Find the total capacitance

→ Do it in stages

◆ $2 \ \& \ 3 \Rightarrow C_{23} = 5 \mu\text{F}$


◆ Add 4 $\Rightarrow C_{234} = 15 \mu\text{F}$

◆ Add 5 $\Rightarrow C_{2345} = 6 \mu\text{F}$

◆ Add 1 $\Rightarrow C_{12345} = 16 \mu\text{F}$

→ Charge supplied by battery (20V)

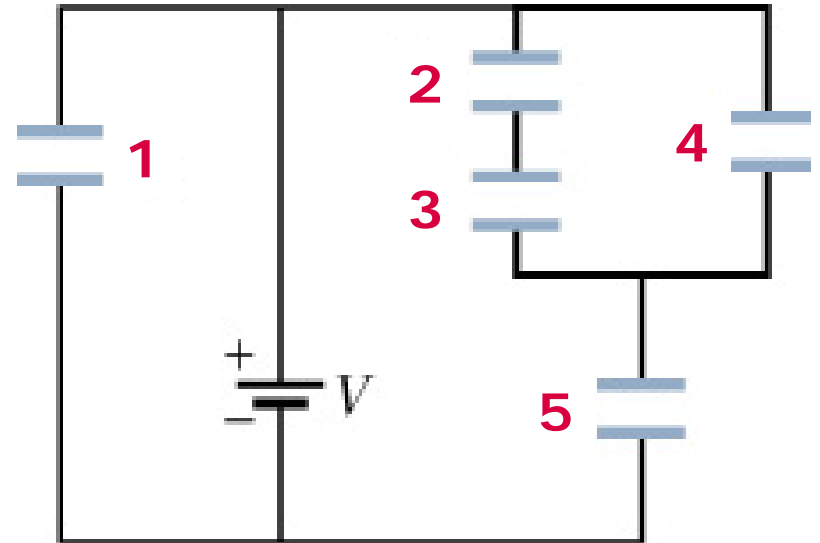◆ $q_{\text{tot}} = C_{12345} \times V = 16 \times 20 = 320 \mu\text{C}$



Find Charges, Voltages on All Capacitors

→ Each capacitor has capacitance $10\mu\text{F}$. $V = 20$ volts

◆ $q_1 = C_1 V = 10 \times 20 = 200\mu\text{C}$

→ $C_{2345} = 6\mu\text{F}$, $q_{2345} = 6 \times 20 = 120 \mu\text{C}$

◆ $q_{2345} = q_{234} = q_5 = 120\mu\text{C}$ (series)

◆ $V_5 = q_5 / C_5 = 120 / 10 = 12$

→ Find q_4 , $V_4 = V_{23}$

◆ $V_{234} = V_4 = 20 - 12 = 8$


◆ $q_4 = C_4 V_4 = 10 \times 8 = 80\mu\text{C}$

→ Find q_2 , q_3 , V_2 , V_3 ($C_{23} = 5\mu\text{F}$)

◆ $q_2 = q_3 = q_{23} = C_{23} \times V_{23} = 5 \times 8 = 40\mu\text{C}$

◆ $V_2 = q_2 / C_2 = 40 / 10 = 4$


◆ $V_3 = q_3 / C_3 = 40 / 10 = 4$

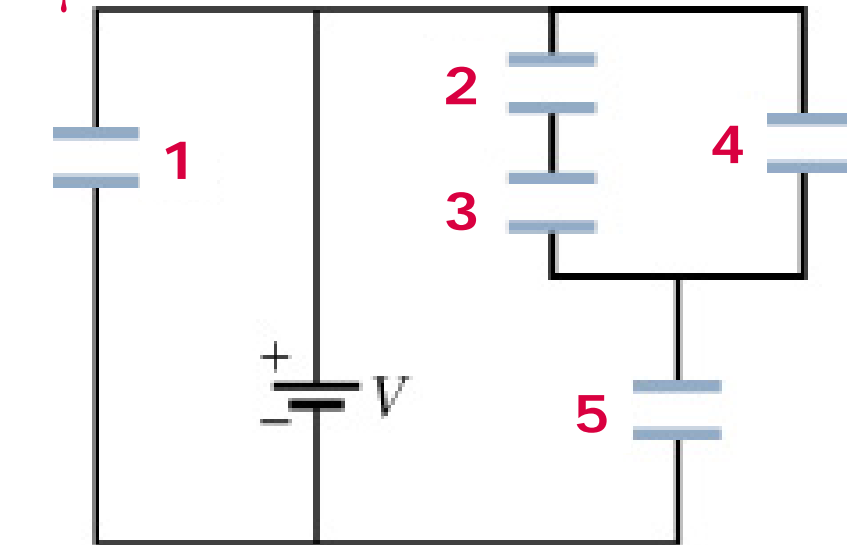

← Check: $V_2 + V_3 = 8 (= V_{23})$


Capacitor Monster

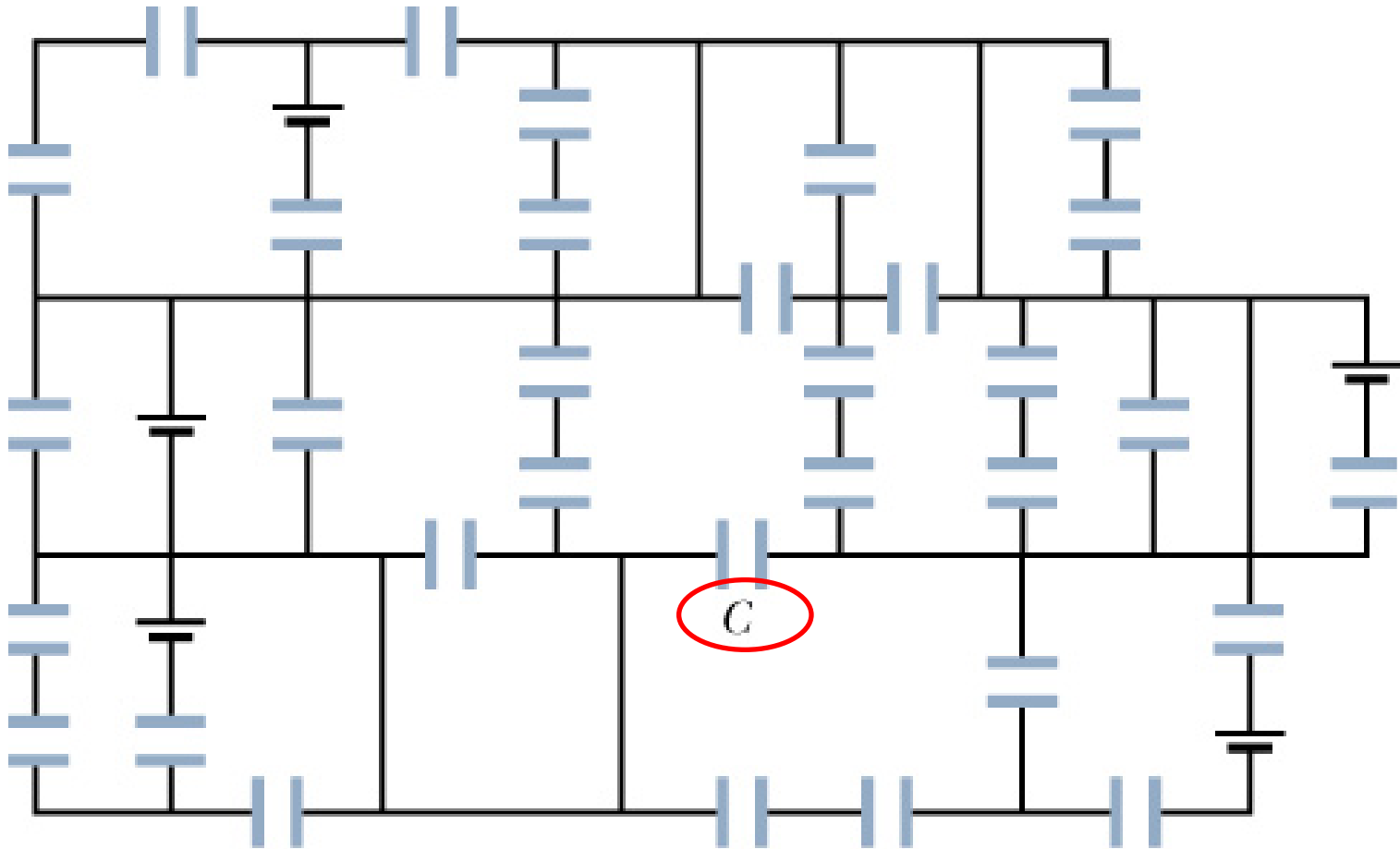All voltages = 4V, all capacitors = $2\mu\text{F}$. What is the charge on C?
Can you find the charge on all capacitors?



Capacitor Monster

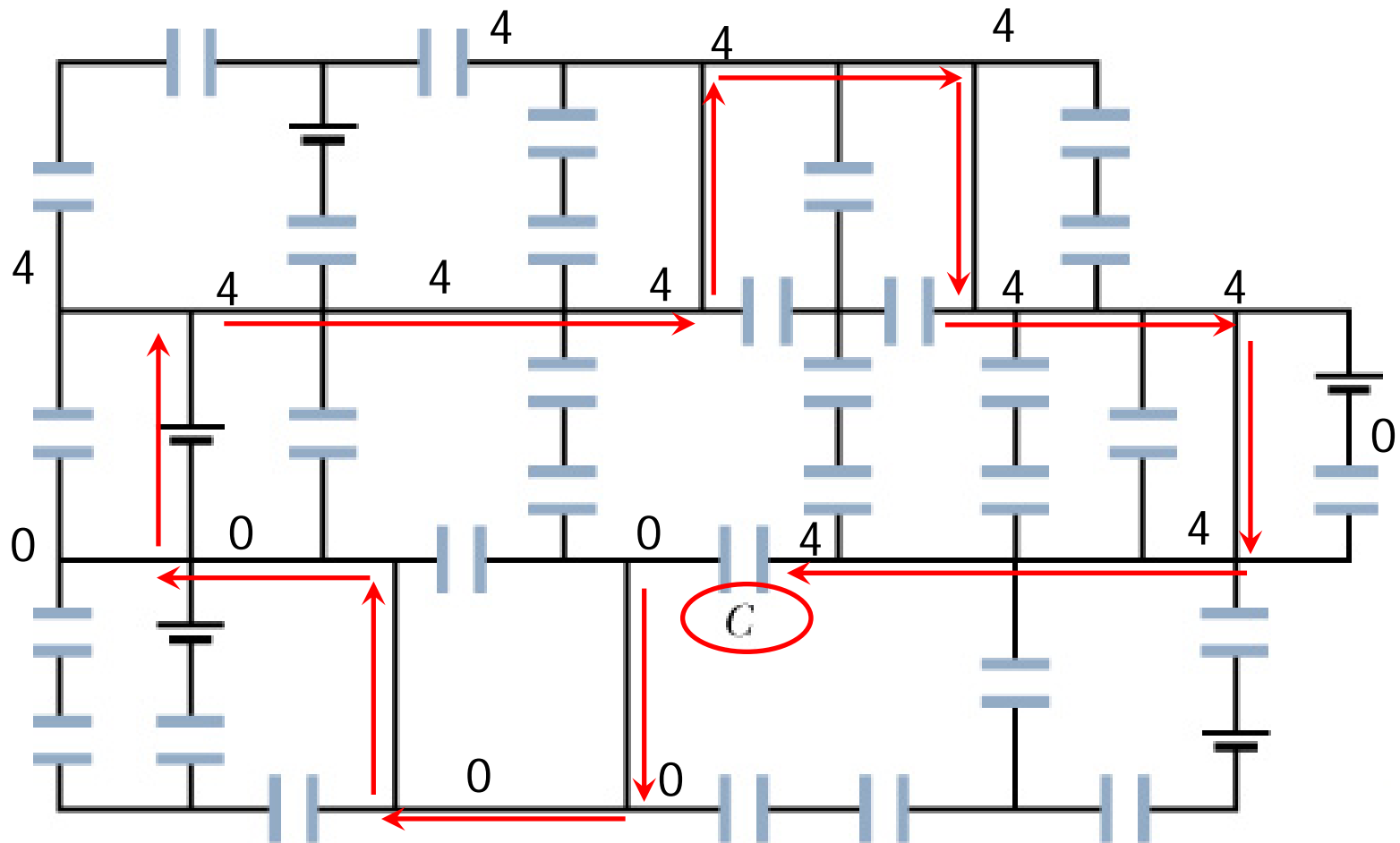All voltages = 4V, all capacitors = $2\mu\text{F}$. What is the charge on C?
 $q = CV = 2 \times 4 = 8\mu\text{C}$



Energy in a Capacitor

- Capacitors have energy associated with them
 - ◆ Grab a charged capacitor with two hands and find out!
- Calculation of stored energy
 - ◆ Proof requires simple calculus derivation
 - ◆ Energy = work moving charge from – to + surface

$$U = \frac{Q^2}{2C} = \frac{1}{2}CV^2$$

- Capacitors store and release energy as they acquire and release charge
 - ◆ This energy is available to drive circuits

Example of Capacitor Energy

→ $C = 5 \mu\text{F}$, $V = 200$

$$U = \frac{1}{2}CV^2 = \frac{1}{2} \times (5 \times 10^{-6}) \times 200^2 = 0.1\text{J}$$

→ Change V to 20000 (as in demo of large HV capacitor)

$$U = \frac{1}{2}CV^2 = \frac{1}{2} \times (5 \times 10^{-6}) \times 20000^2 = 1000\text{J}$$

Where is the Energy Stored?

→ Answer: Energy is stored in the electric field itself!!

→ Example: Find energy density of two plate capacitor

◆ E field is constant

$$u = \frac{U}{Ad} = \frac{CV^2}{2Ad} = \frac{\epsilon_0 (A/d)(Ed)^2}{2Ad} = \frac{1}{2} \epsilon_0 E^2$$

→ Energy density depends only on E field!


◆ A general result, independent of geometry

◆ Can be shown more generally by Maxwell's equations

$$u = \frac{1}{2} \epsilon_0 E^2$$

Dielectric Materials and Capacitors

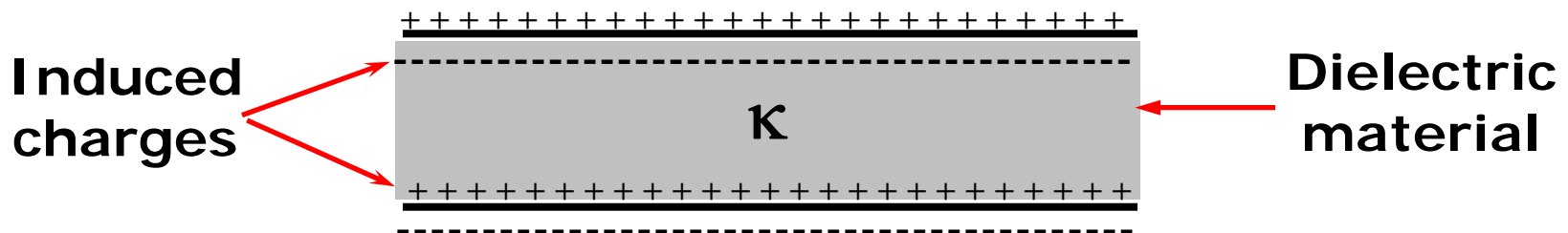→ Insulating material that can be polarized in E field




→ Induced charges at dielectric surface partially cancel E field

- ◆ $E \rightarrow E / \kappa$ $\kappa > 1$ is "dielectric constant"
- ◆ $V \rightarrow V / \kappa$ (since $V = Ed$)
- ◆ $C \rightarrow \kappa C$ (since $C = Q / V$)


→ But "good" dielectric requires more than high κ value

- ◆ Good insulator (no charge leakage)
- ◆ High breakdown voltage (no arcing at high voltage)
- ◆ Low cost (affordable)

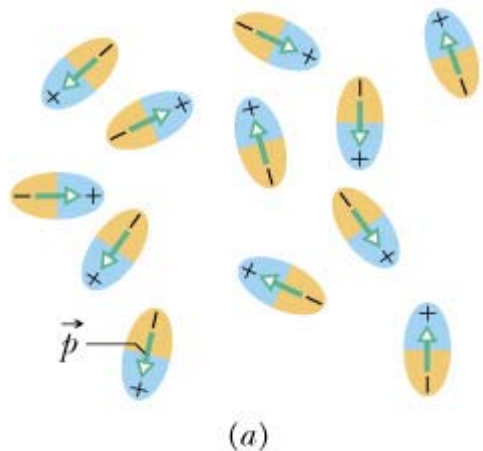Dielectric Mechanism is Due to Polarization



$E = 0$, Dipoles randomly aligned

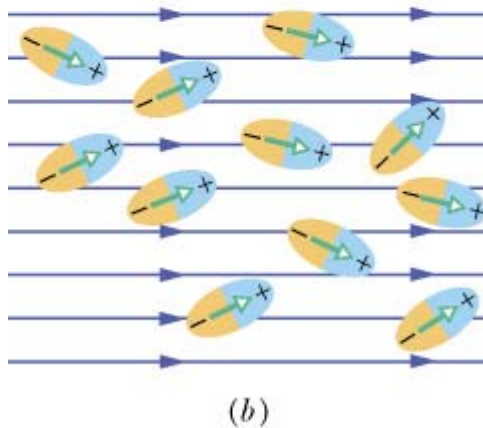

- **E applied, partially aligns dipoles**
- **Aligned dipoles induce surface charges**
- **Surface charges partially cancel E field**

<http://hyperphysics.phy-astr.gsu.edu/hbase/electric/dielec.html>

Dielectric Constants of Some Materials

Material	Dielectric constant κ
Vacuum	1.0
Air	1.00059
Bakelite	4.9
Strontium titanate	310
Water	80
Ethanol	24
Mica	5.4
Barium Titanate	100 – 1250
Paper	3.7
Beeswax	2.7 – 3.0
Silica glass	3.8

Example of Dielectric Use

→ Simple capacitor: $A = 2\text{m}^2$, $d = 1\mu\text{m}$ (no dielectric)

◆ Place 200 volts across C

$$C = \epsilon_0 \frac{A}{d} = 8.85 \times 10^{-12} \frac{2}{10^{-6}} = 1.77 \times 10^{-5} = 17.7 \mu\text{F}$$

$$q = CV = 17.7 \mu\text{F} \times 200 = 3540 \mu\text{C}$$

$$U = \frac{1}{2} CV^2 = \frac{1}{2} (1.77 \times 10^{-5}) (200)^2 = 0.35 \text{ J}$$

→ Now disconnect C from circuit

◆ Insert strontium titanate dielectric ($\kappa = 310$) into capacitor

◆ Charge is conserved, calculate new C, V and U

$$C_{\text{new}} = \kappa C = 310 \times 17.7 = 5490 \mu\text{F}$$

$$V_{\text{new}} = V / \kappa = 200 / 310 = 0.65 \text{ volts}$$

$$U_{\text{new}} = U / \kappa = 0.35 / 310 = 0.0011 \text{ J} \quad \left(= \frac{1}{2} C_{\text{new}} V_{\text{new}}^2 \right)$$

Similar Example

→ Same capacitor as before, but this time insert dielectric while C is in the circuit

◆ $C_{\text{new}} = \kappa C = 5490 \mu\text{F}$

◆ V is still 200 volts (maintained by battery)

→ Calculate new q and U in this example

$$q_{\text{new}} = C_{\text{new}} V = 5490 \mu\text{F} \times 200 = 1.1 \text{ C}$$

$$U_{\text{new}} = \frac{1}{2} C_{\text{new}} V^2 = \frac{1}{2} (5490 \times 10^{-6}) (200)^2 = 110 \text{ J}$$


→ Notice how q and U are increased by factor κ

ConcepTest

→ Two identical capacitors are given the same charge Q , then disconnected from a battery.

After C_2 has been charged and disconnected it is filled with a dielectric. Compare the voltages of the two capacitors.

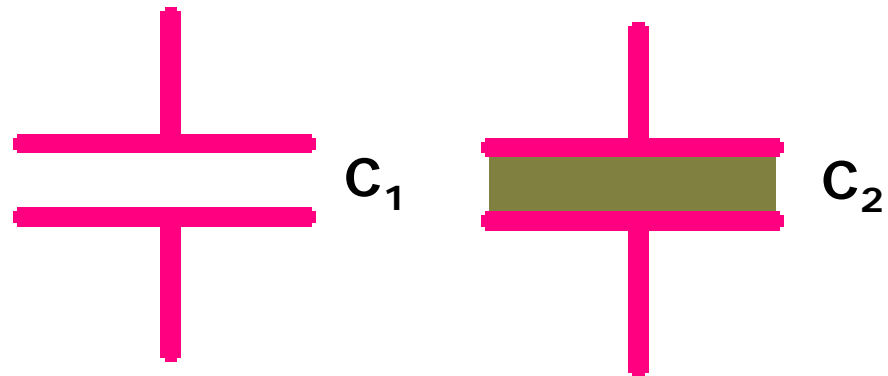- ◆ (1) $V_2 < V_1$
- ◆ (2) $V_2 > V_1$
- ◆ (3) $V_2 = V_1$



Charge is unchanged, but dielectric reduces E to E/κ and V to V/κ


ConcepTest

→ When we fill the capacitor with the dielectric, what is the amount of work required to fill the capacitor?

◆ (1) $W > 0$

◆ (2) $W < 0$

◆ (3) $W = 0$

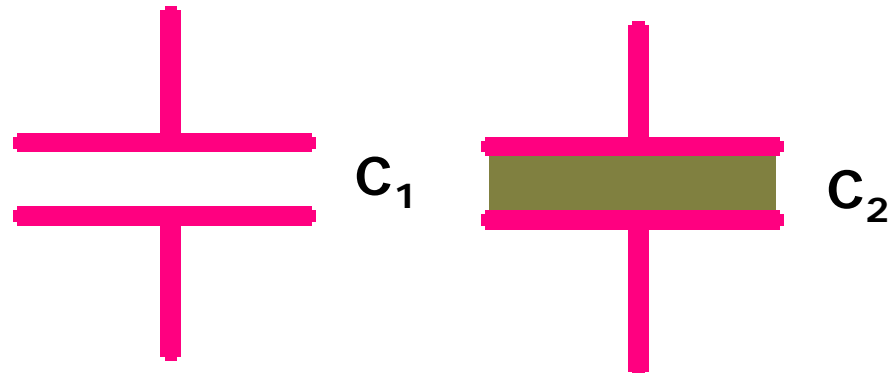

Energy is reduced from U to U/κ , so work is negative

If U is total energy in capacitor

- | | | |
|------------------|---------------------------------|----------------|
| ➤ Positive work: | One "pushes in" dielectric | $\Delta U > 0$ |
| ➤ Negative work: | Capacitor "sucks in" dielectric | $\Delta U < 0$ |