

Instructor(s): *Profs. P. Kumar, Z. Qiu*PHYSICS DEPARTMENT
Exam 1

September 26, 2013

PHY 2054

Name (print, last first): _____ Signature: _____

*On my honor, I have neither given nor received unauthorized aid on this examination.***YOUR TEST NUMBER IS THE 5-DIGIT NUMBER AT THE TOP OF EACH PAGE.**


- (1) **Code your test number on your answer sheet (use lines 76–80 on the answer sheet for the 5-digit number).** Code your name on your answer sheet. **DARKEN CIRCLES COMPLETELY.** Code your UFID number on your answer sheet.
- (2) Print your name on this sheet and sign it also.
- (3) Do all scratch work anywhere on this exam that you like. **Circle your answers on the test form.** At the end of the test, this exam printout is to be turned in. No credit will be given without both answer sheet and printout.
- (4) **Blacken the circle of your intended answer completely, using a #2 pencil or blue or black ink.** Do not make any stray marks or some answers may be counted as incorrect.
- (5) Hand in the answer sheet separately.

Useful Constants:

$k = 9 \times 10^9 \text{Nm}^2/\text{C}^2$			$\epsilon_0 = 8.85 \times 10^{-12} \text{C}^2/(\text{Nm}^2)$	
electron charge = $-1.6 \times 10^{-19} \text{C}$			electron mass = $9.11 \times 10^{-31} \text{kg}$	
V=volt	N=newton	J=joule	m="milli"= 10^{-3}	C=coulomb
k="kilo"= 10^3	"pico"= 10^{-12}	n="nano"= 10^{-9}	proton charge = $+e$	proton mass = $1.67 \times 10^{-27} \text{kg}$
μ ="micro"= 10^{-6}		$g = 9.8 \text{ m/s}^2$		M="mega"= 10^6

1. If
- $\mathcal{E} = 18.0 \text{ V}$
- , what is the current in the
- $15\text{-}\Omega$
- resistor?

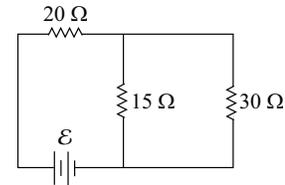- (1) 0.40 A
- (2) 0.60 A
- (3) 0.20 A
- (4) 0.52 A
- (5) 1.00 A




2. A
- 12.0 V
- battery is placed across a
- $4.00 \text{ }\Omega$
- resistor. If the current through the resistor is
- 2.80 A
- , what is the terminal voltage of the battery?

- (1) 11.2 V
- (2) 12.8 V
- (3) 11.6 V
- (4) 12.0 V
- (5) 9.6 V

3. Four
- $12 \text{ }\Omega$
- resistors are connected together. Which of the following resistances cannot be formed using all 4 resistors?


- (1) 60Ω
- (2) 9.0Ω
- (3) 12Ω
- (4) 48Ω
- (5) 20Ω

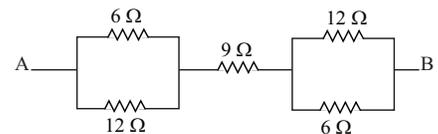4. What is the resistance of the combination of resistors?



- (1) 17Ω
- (2) 25Ω
- (3) 8.0Ω
- (4) 34Ω
- (5) 4.0Ω

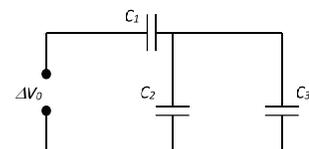
5. If
- $C_1 = 25\mu\text{F}$
- ,
- $C_2 = 20\mu\text{F}$
- ,
- $C_3 = 10\mu\text{F}$
- , and
- $\Delta V_0 = 42 \text{ V}$
- , determine the energy stored by
- C_2
- .



- (1) 3.6 mJ
- (2) 1.3 mJ
- (3) 1.6 mJ
- (4) 2.9 mJ
- (5) 2.2 mJ

6. If $R_1 = 6\Omega$, $R_2 = 8\Omega$, $R_3 = 2\Omega$, $\mathcal{E}_1 = 8\text{ V}$, and $\mathcal{E}_2 = 28\text{ V}$, what is the current in R_2 ?

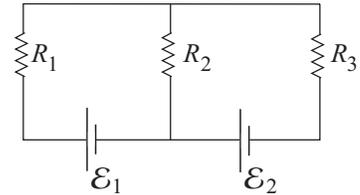(1) 2 A
 (2) 4 A
 (3) 6 A
 (4) 8 A
 (5) 10 A




7. If a 2.0 pF capacitor has a voltage of 20 mV, how many more electrons are on the negative plate than on the positive plate?

(1) 0.5×10^6 (2) 2.5×10^5 (3) 4.0×10^{14} (4) 2.0×10^3 (5) none, the electrons are in equal numbers on the plates.

8. If protons are accelerated from rest in a Van de Graff accelerator through a potential difference of 1.00 MV, what is their resulting speed?

(1) $1.38 \times 10^7\text{ m/s}$ (2) $6.25 \times 10^7\text{ m/s}$ (3) $9.79 \times 10^6\text{ m/s}$ (4) $3.67 \times 10^8\text{ m/s}$ (5) $6.92 \times 10^6\text{ m/s}$

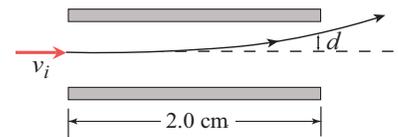9. A horizontal beam of electrons initially moving at $3.9 \times 10^7\text{ m/s}$ is deflected vertically up by the vertical electric field between oppositely charged parallel plates. The magnitude of the field is $2.30 \times 10^4\text{ N/C}$. What is the vertical deflection d of the positrons as they leave the plates?



(1) 0.531 mm (2) 1.5 mm (3) 3.5 mm (4) 6.3 mm (5) 0.153 mm

10. A copper wire of length l and radius r has resistance R . The wire is pulled hard so that its length is tripled, although its density remains unchanged. What is its resistance now?

(1) $9R$ (2) $3R$ (3) $R/3$ (4) $R/9$ (5) none of these

11. A capacitor is attached across a battery and charged. Then the battery is removed leaving the capacitor charged. The positive lead of the capacitor is then connected to one lead of a previously uncharged identical capacitor, and then the other lead of the charged capacitor is connected to the other lead of the second capacitor. How does the energy E_o stored in the originally charged capacitor compare to the energy E_f stored in the connected capacitors?

(1) $E_o = 2E_f$ (2) $E_o < E_f$ (3) $E_o = E_f$ (4) $E_o = 4E_f$ (5) none of these

12. Two small, positively charged spheres have a combined charge of $50\ \mu\text{C}$. If each sphere is repelled from the other by an electrostatic force of 1N when the spheres are 2.0 m apart, what is the charge (in μC) on the sphere with the smallest charge?


(1) 11.6 (2) 1.2 (3) 25 (4) 19.8 (5) none of these

13. Two charges, $q_1 = -1\text{ C}$ and $q_2 = -4\text{ C}$, are placed along the x-axis a distance L apart with charge q_1 at the origin and q_2 at $x = L$. A third charge, $q_3 = +4/9\text{ C}$, is also placed along the x-axis such that there is no net Coulomb force on any of the charges. What is the position of this charge along the x axis in units of L , *i.e.*, what is x/L ?

(1) $\frac{1}{3}$ (2) $\frac{1}{2}$ (3) 1 (4) 2 (5) 3

22. The capacitance across A and B is $1.563\mu\text{F}$. What is the capacitance C in μF ?

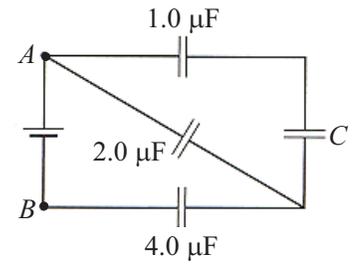- (1) 1.3
- (2) 3.4
- (3) 10.5
- (4) 56
- (5) none of these



THE FOLLOWING QUESTIONS, NUMBERED IN THE ORDER OF THEIR APPEARANCE ON THE ABOVE LIST, HAVE BEEN FLAGGED AS CONTINUATION QUESTIONS: 21 FOLLOWING GROUPS OF QUESTIONS WILL BE SELECTED AS ONE GROUP FROM EACH TYPE

- TYPE 1
 Q# S 15
 Q# S 16
 Q# S 17