
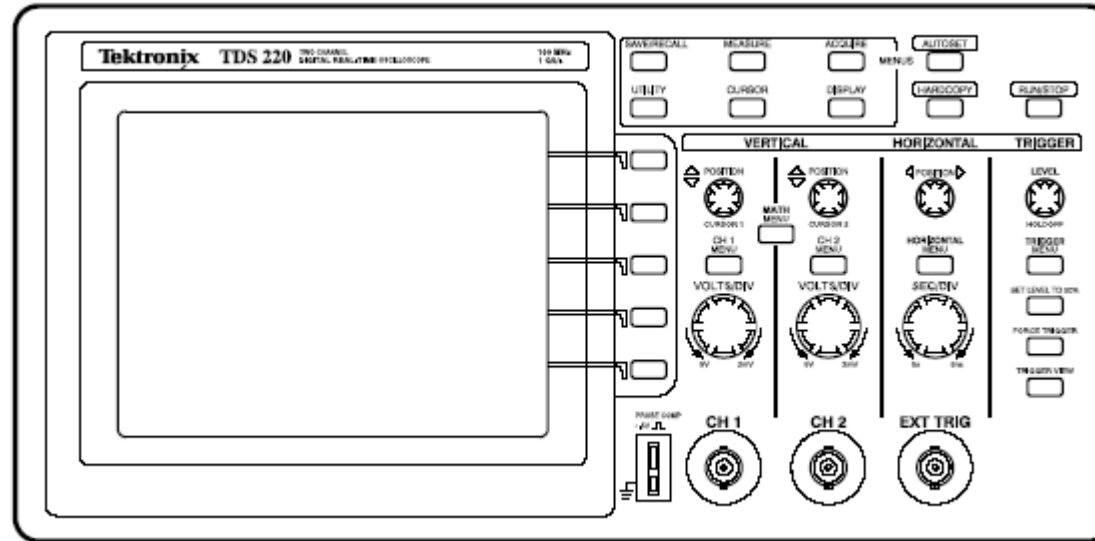


# *Introduction to oscilloscopes*

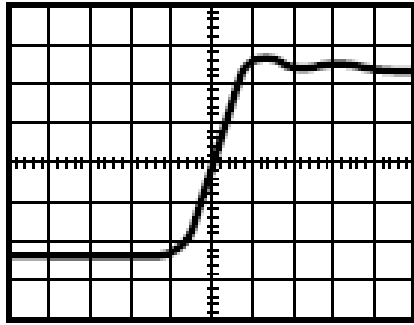


- *Triggering*
- *10x probes*
- *DC coupling vs AC coupling*
- *X-Y mode*


# Triggering



Triggered waveform

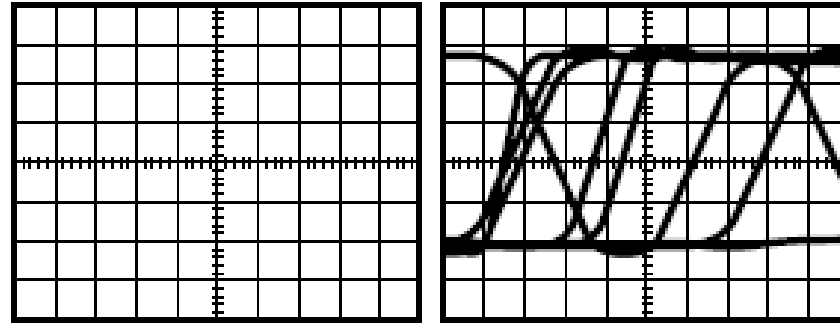

Untriggered waveforms

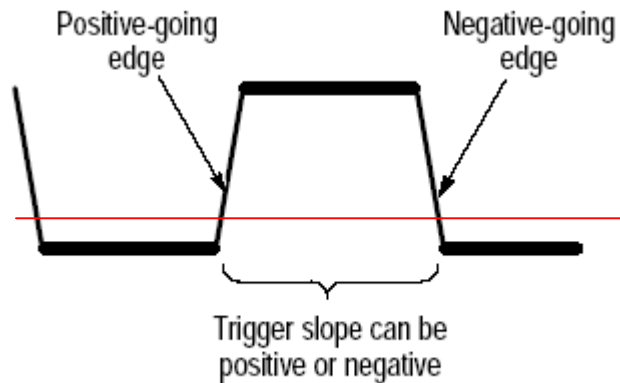

*Trigger Slope:*

*Positive/negative: rising or falling edge*

*Trigger mode:*

*Normal: stops if cannot detect trigger*

*Auto: keeps going even if cannot detect trigger*

*Single: run/stop button*

*Trigger source:*

*Ch 1*



*Ch 2*

*Ext/Ext 5*

*Line:*


# Triggering

$$y = \sin(t) + 0.4\cos(10t)$$

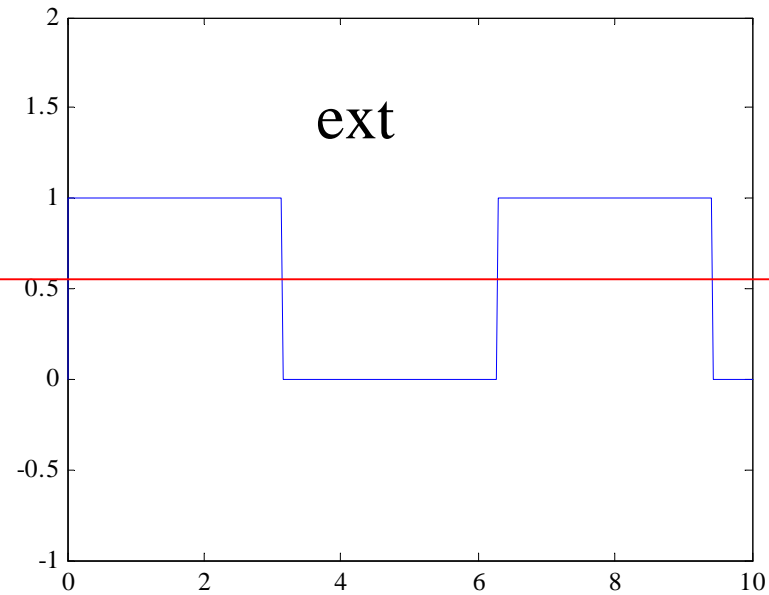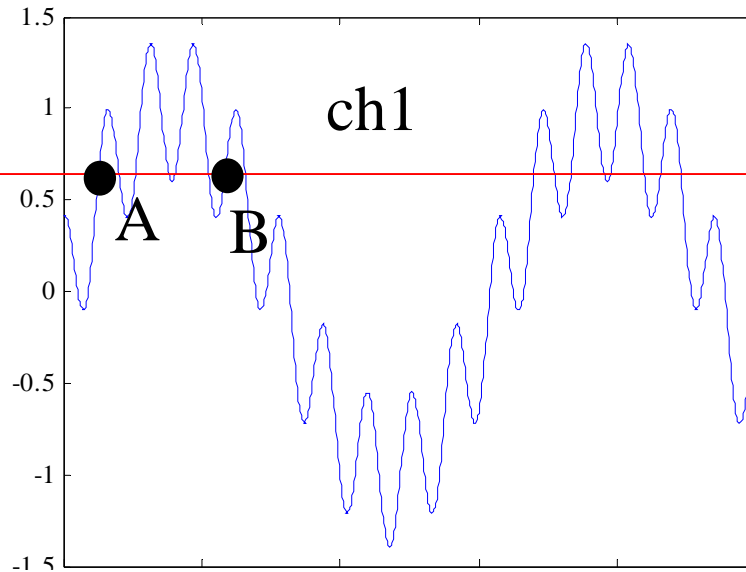


*The “sync” output of function generator provides a clean square wave at the same frequency as the output*

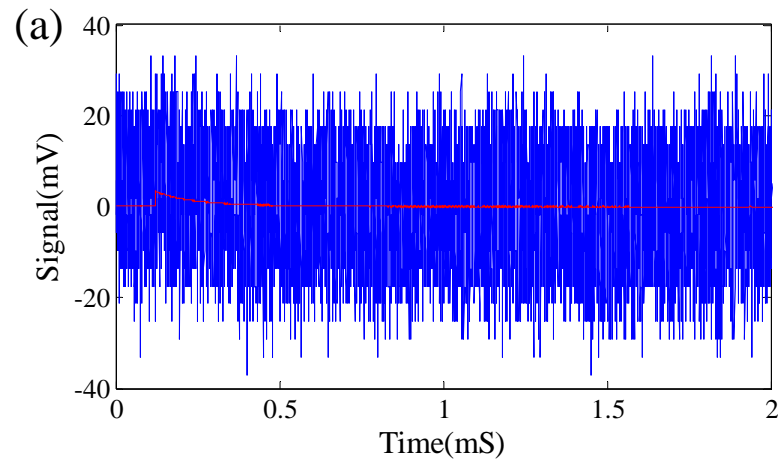*Importance of external trigger:  
recovering signal from noise by averaging*





Blue = a single trace

Red = 262144 averages


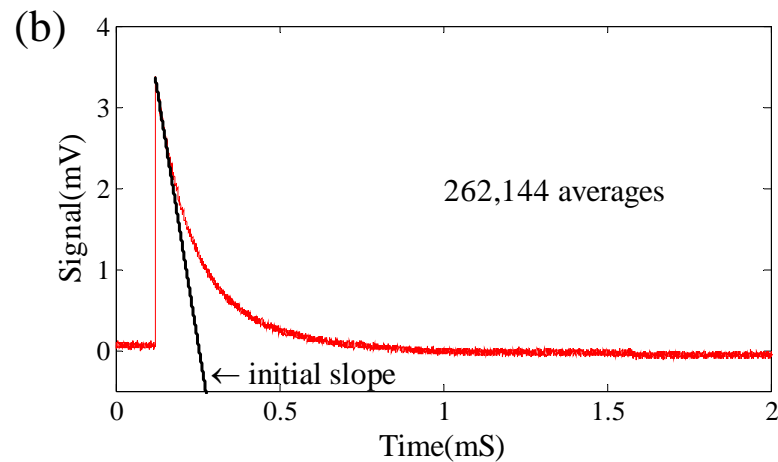


# Coupling: DC vs AC

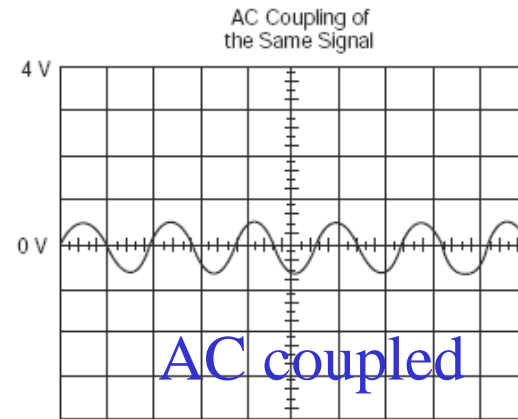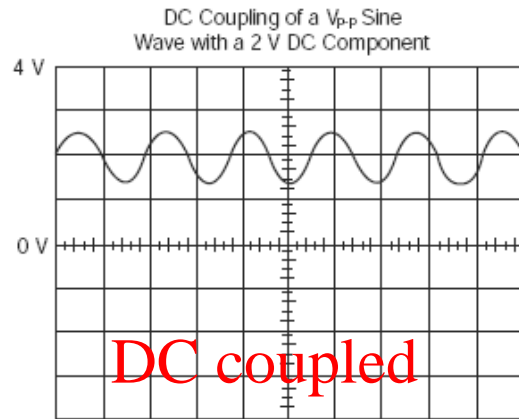

*Removes all DC information*

*To observe small AC on top of large DC*

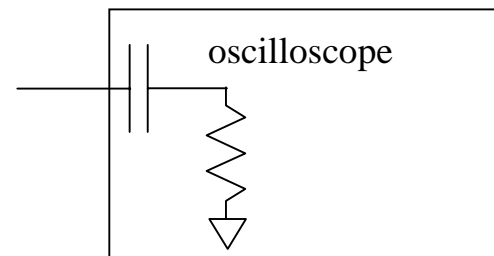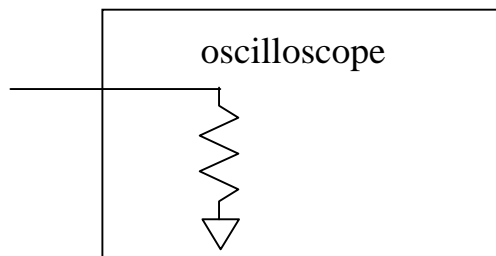



$$z_c = 1/j\omega C \quad f_{3db} = 1/2\pi RC$$

# Coupling: DC vs AC


*Low frequency waveforms can be severely distorted by the high pass filter*

*AC coupled*

*DC coupled*

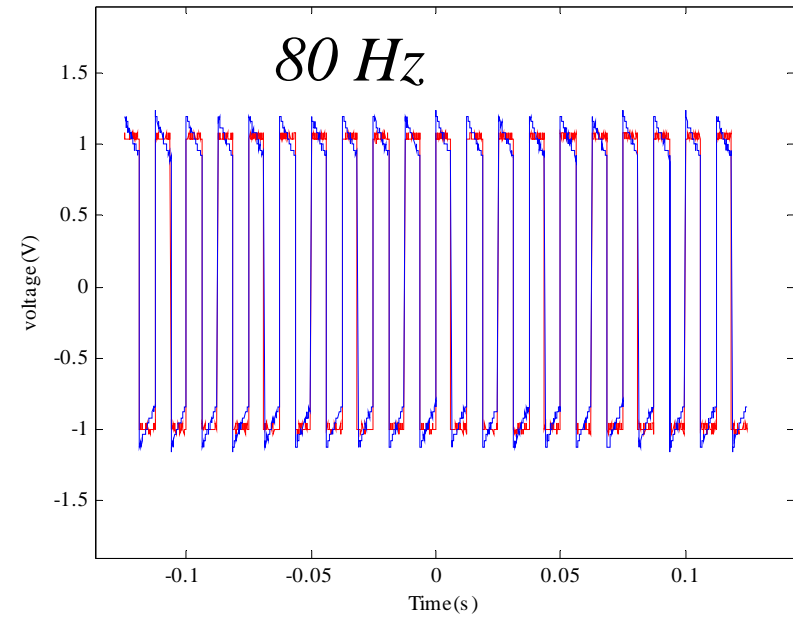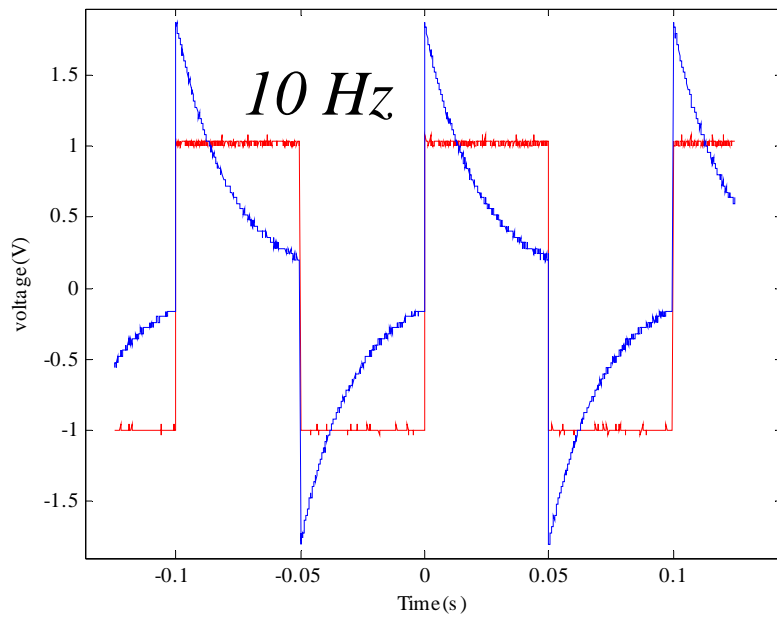



# Oscilloscope probes

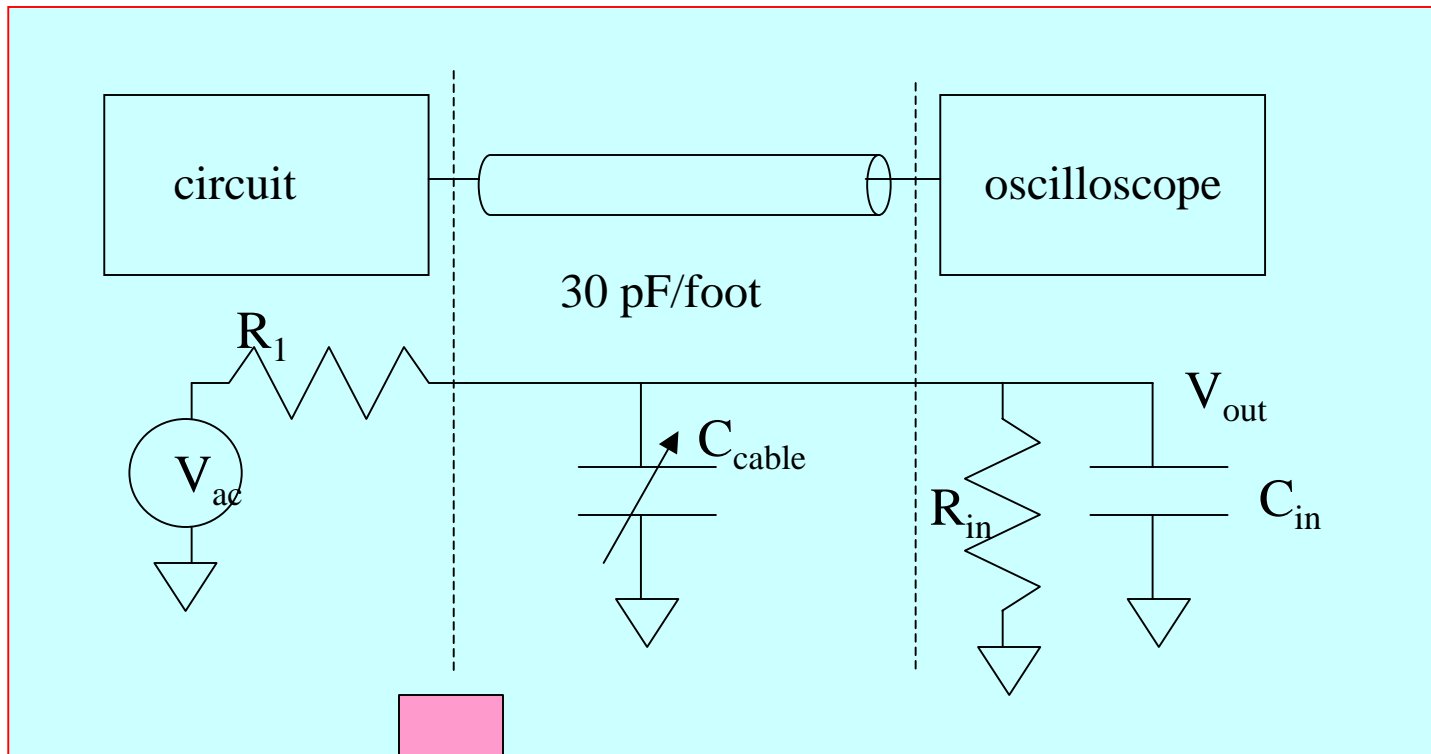

*For scope:*




$$R_{in} = 1\text{ M}$$

$$C_{in} \sim 20\text{ pF}$$

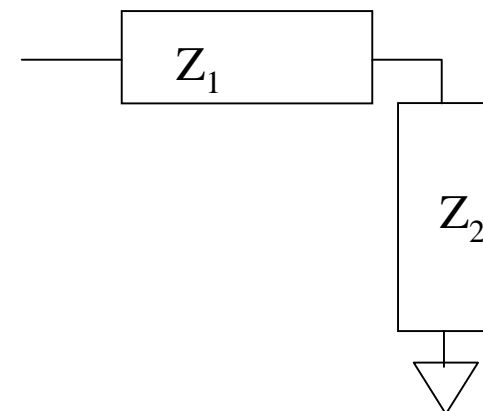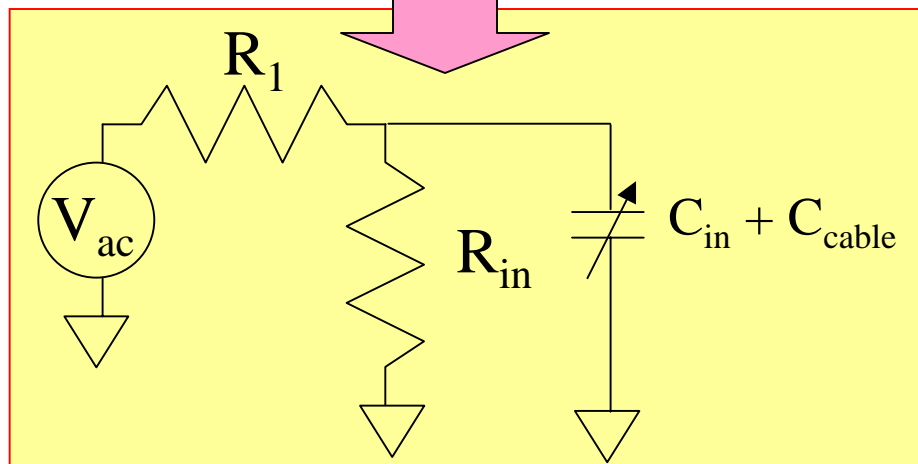

*$Z_1$  and  $Z_2$  are frequency dependent and changes for each circuit*
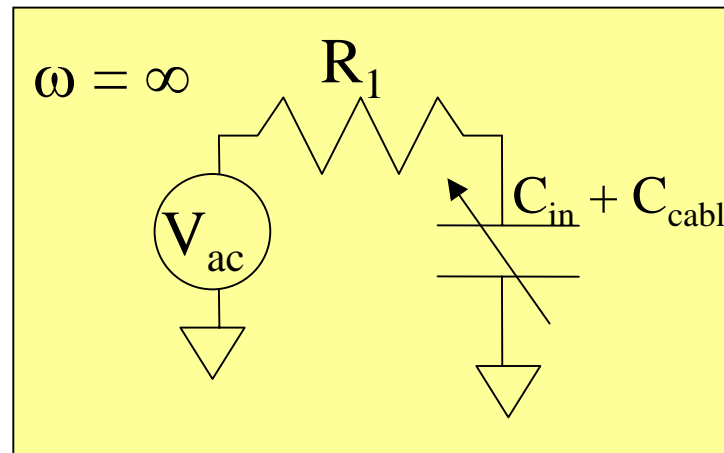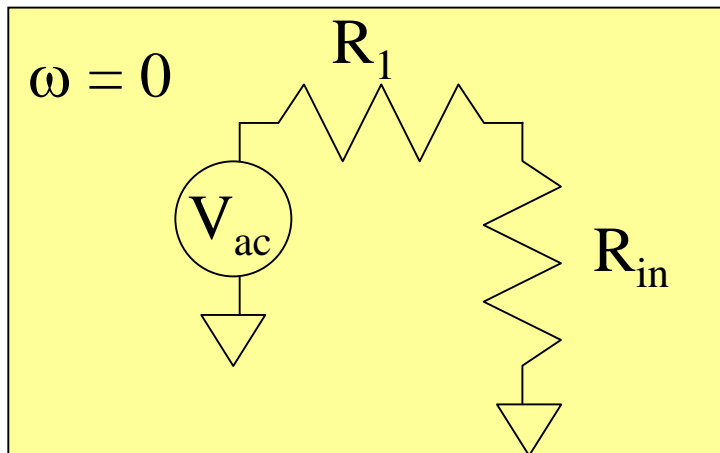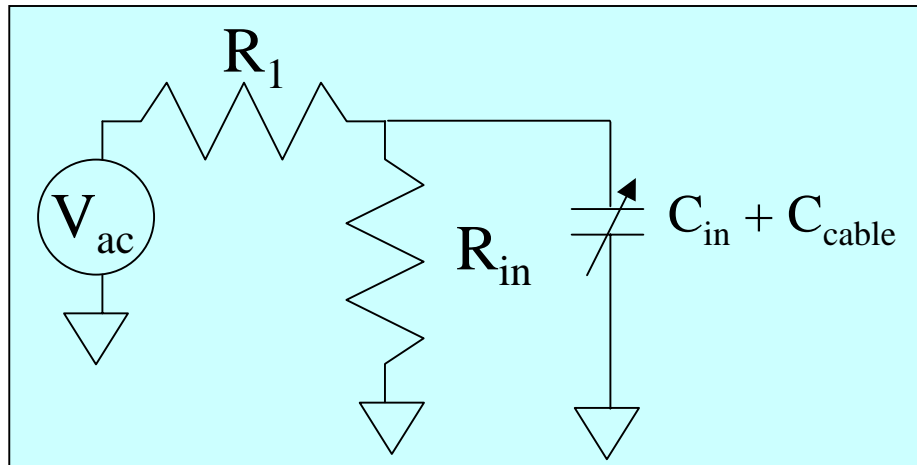
# Oscilloscope impedance and stray capacitance can load the circuit




*Example:*

$$R_1 = 10k$$

$$C = 50 \text{ pF}$$

$$f_{3db} = 1/2\pi RC$$

$$= 320 \text{ kHz}$$

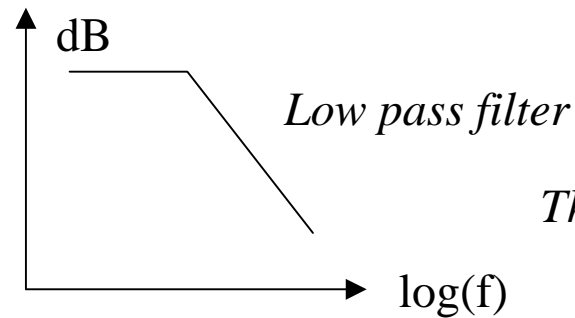


*The signal is distorted!*




## *Advantages of 10x probe*

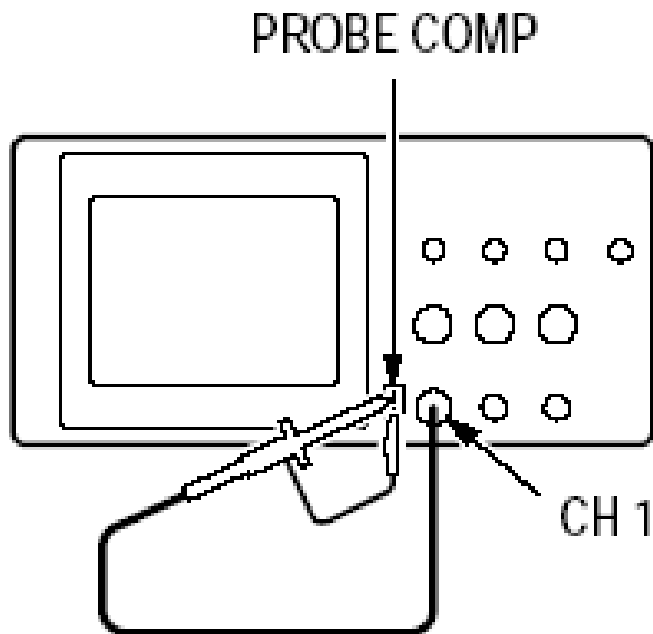- 1. Input impedance 10 times larger (reduce loading)*
- 2. Frequency independent (almost, if tuned correctly)*





## Resistive part:

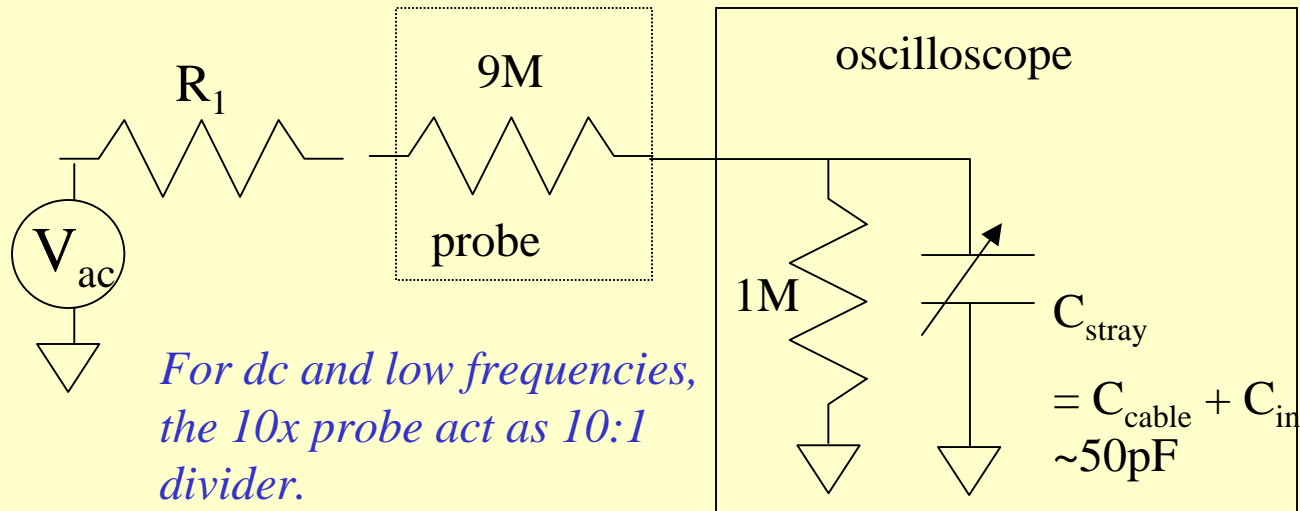


## How to eliminate frequency dependence?

Add capacitor to probe

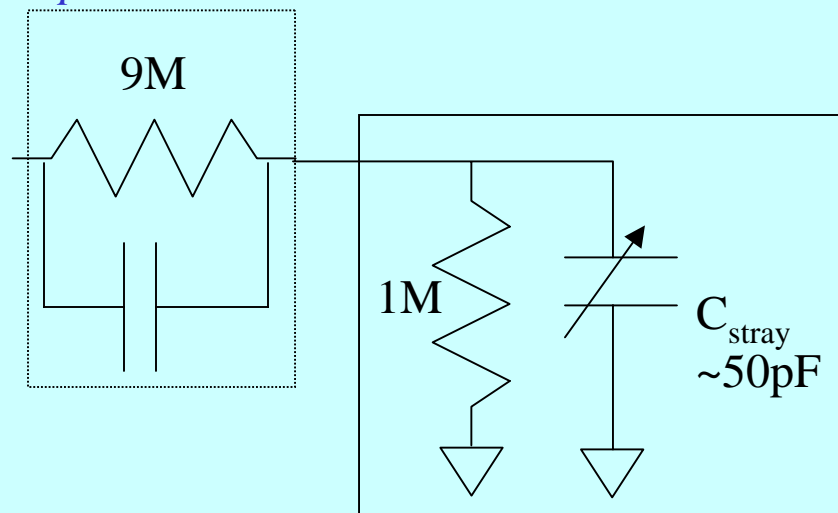

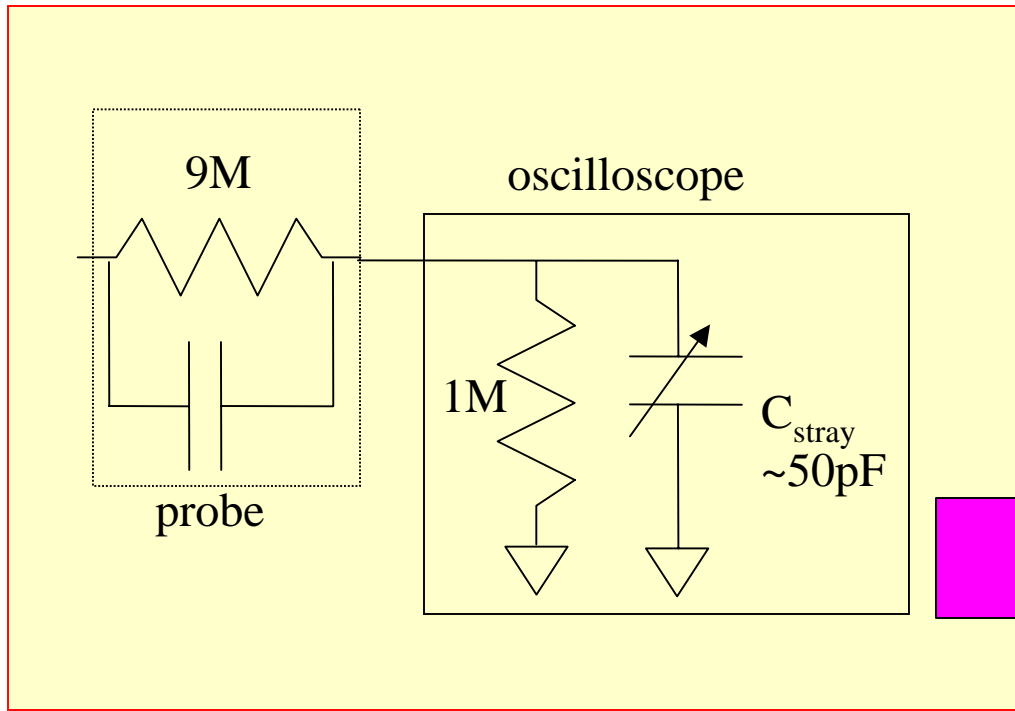


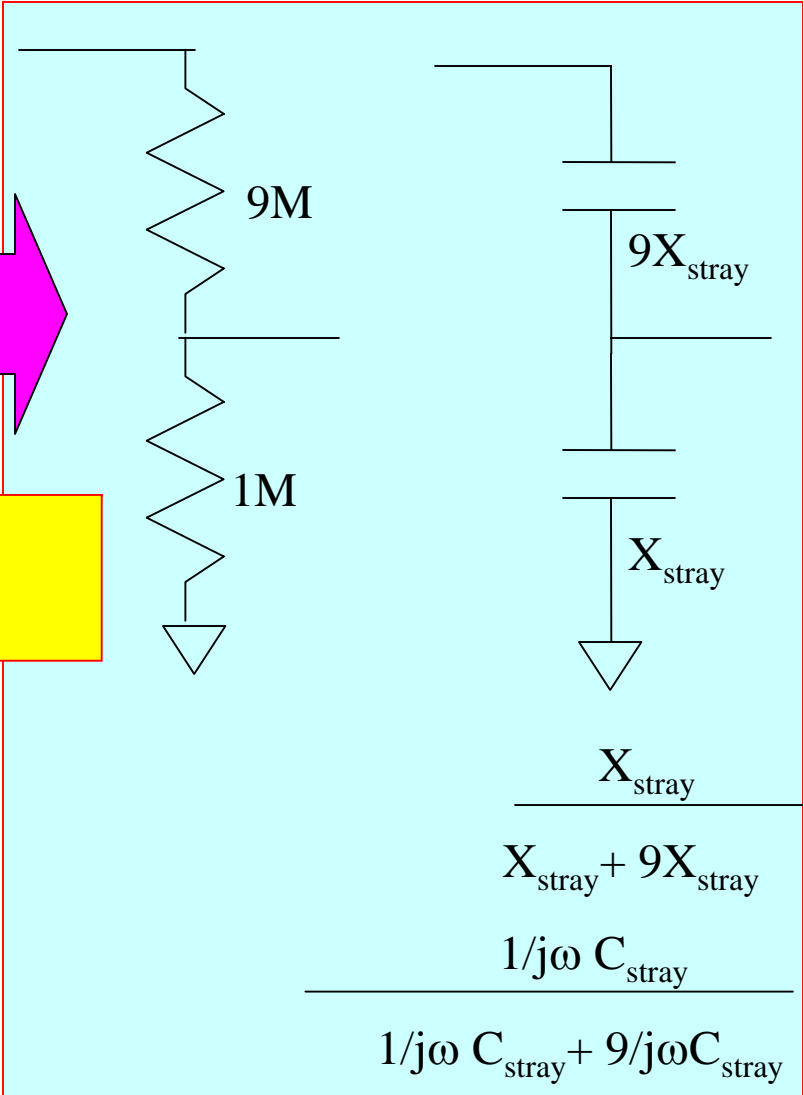*Consider the resistive and capacitive parts separately*





*Both dividers are 1:10, independent of frequency  
They give the same output voltage*

*Remember  
Quiz 1:*

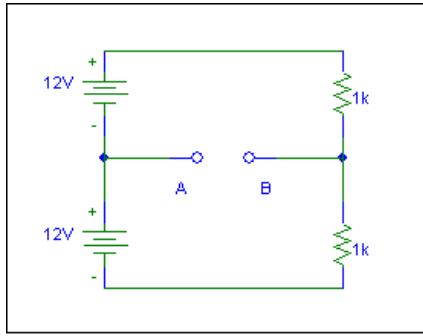

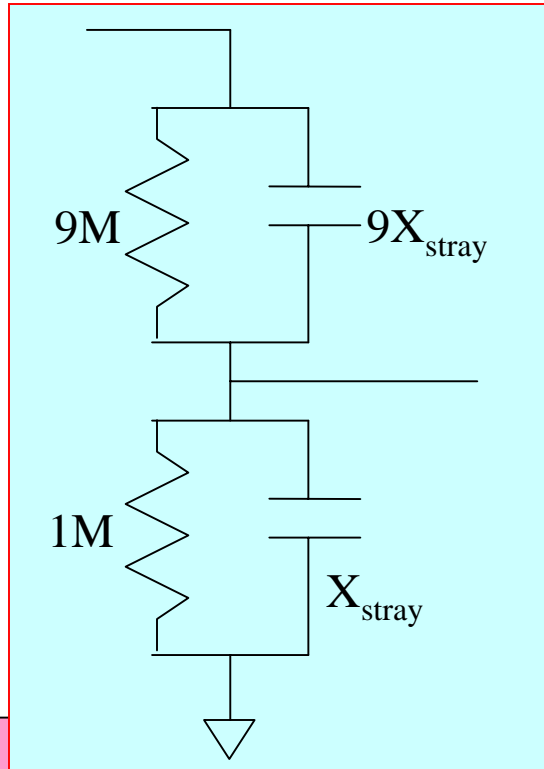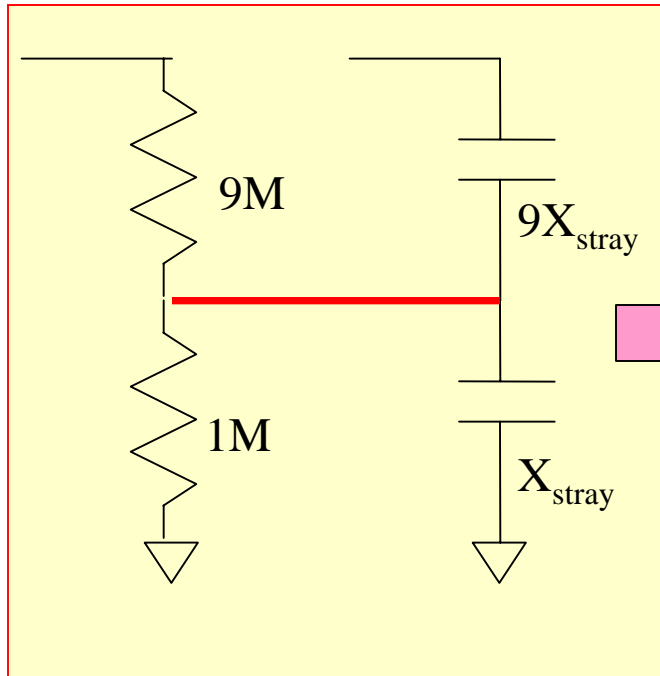
Both dividers give the *same* output voltage → can join the output



$$X_c = 1/j\omega C$$

$$C_{\text{probe}} \sim 50\text{pF}/9 \\ = 5.6 \text{ pF}$$

$$C_{\text{stray}} \sim 50\text{pF}$$

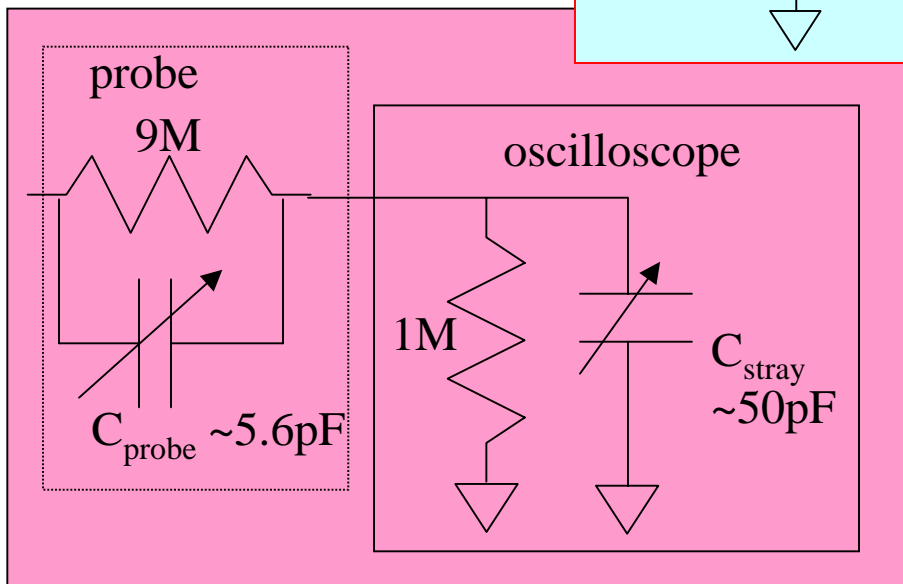



*10x probe divides signal by 10. To display the actual signal, we need to tell the scope to multiply its measurement by 10.*

## Tuning the probe


The oscilloscope provides a square wave output on its front panel, labeled as “probe adjust”

A square wave can be Fourier decomposed into a sum of many frequencies.

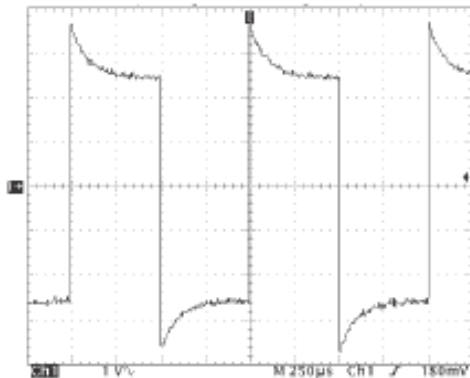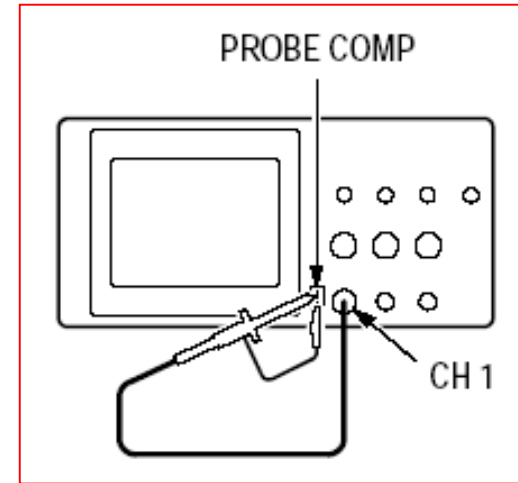
If the probe and scope attenuates all frequencies by 10, we should get back a square wave.



a. Overcompensated.

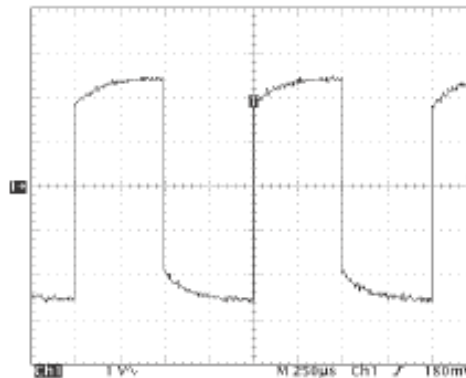


b. Under compensated.

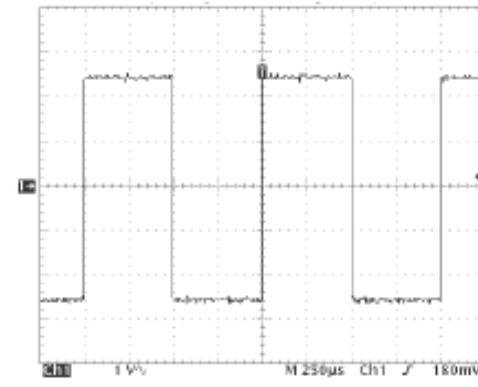

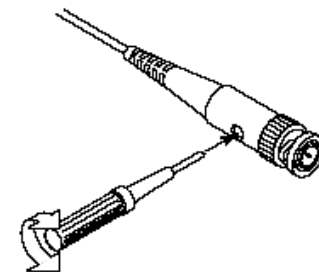c. Properly compensated.

Tune probe capacitance until the scope shows a good square wave.



## Display:

*YT: displays Ch1 and/or Ch2 as a function of time*



*XY: displays Ch1 as a function of Ch 2*

$$x(t) = A \cos(\omega_1 t - \delta_1)$$
$$y(t) = B \cos(\omega_2 t - \delta_2)$$

Example:

$$\omega_1 = \omega_2, \delta_1 = \delta_2$$



$$y = B/A x$$

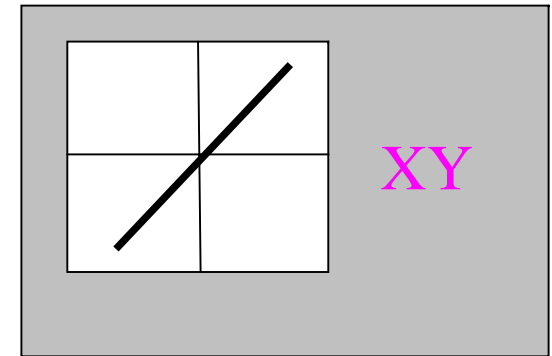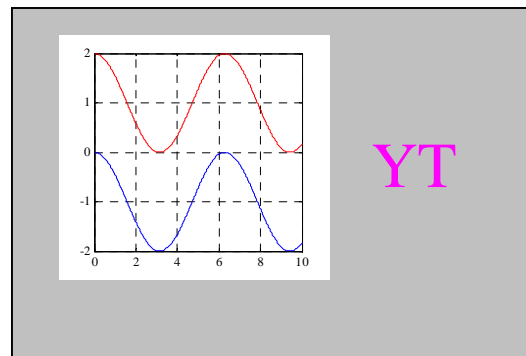

$$\omega_1 = \omega_2, \delta_2 = 0, \delta_1 = \pi/2$$

$$x(t) = A \cos(\omega_1 t)$$


$$y(t) = B \sin(\omega_1 t)$$

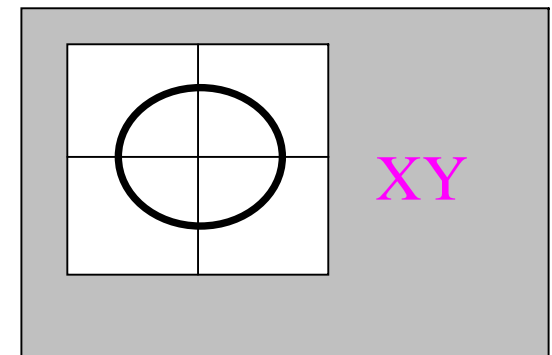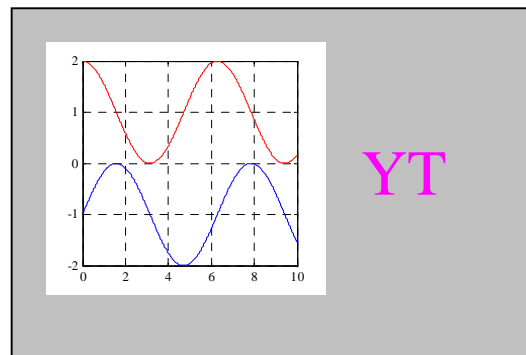


# Lissajous Curves

$$x(t) = A \cos(\omega_1 t - \delta_1)$$

$$y(t) = B \cos(\omega_2 t - \delta_2)$$

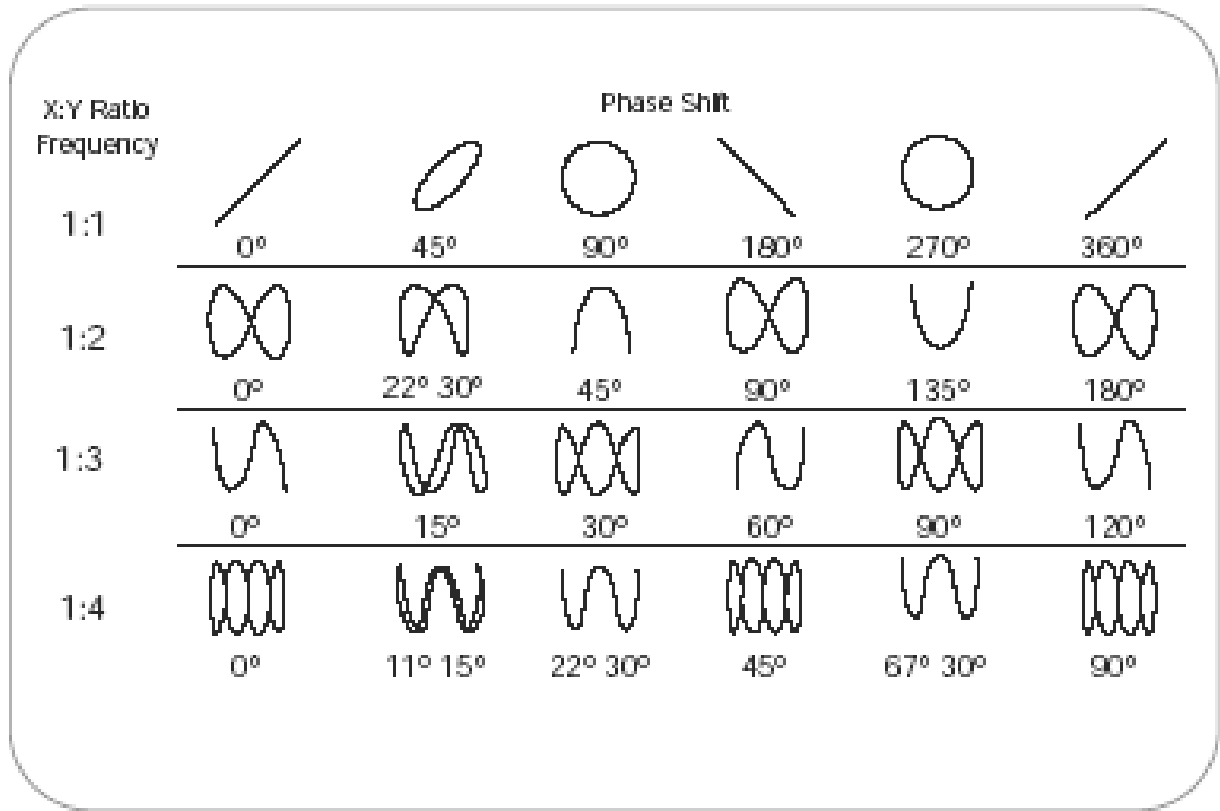

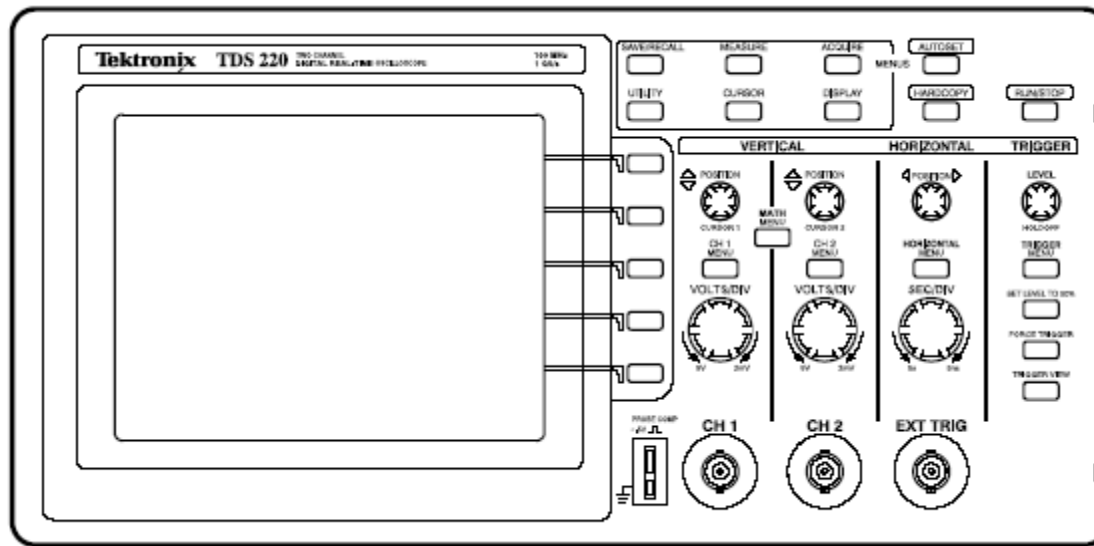

### *Checklist for oscilloscope operation*

- 1. Make sure probe compensation is set to the correct value (1x, 10x)*
- 2. If you cannot get signal on screen, press “autoscale”*
- 3. Check DC/AC coupling*
- 4. Check trigger source*