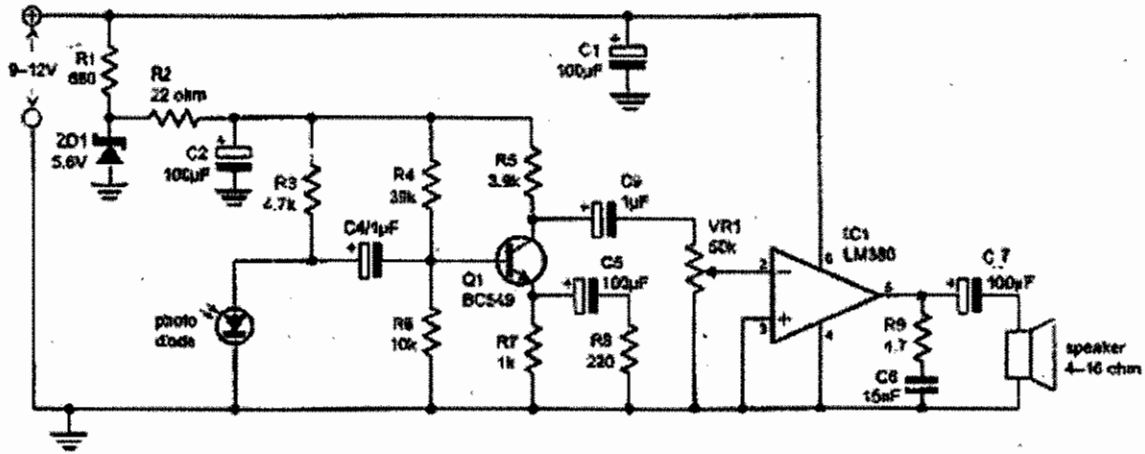




## The Receiver



This is the circuit for the receiver, where light from the transmitter is detected and converted to a voltage by the photodiode. The signal is amplified by Q1 and IC1, which drives the speaker.