

LOW TEMPERATURE TRANSFORMER READOUT ELECTRONICS Flavio Gatti

UNIVERSITY and INFN of Genoa, Italy

Luigi Parodi, Maria Ribeiro Gomes, Lorenza Ferrari, Riccardo Valle, Simeone Dussoni, Adriano Bevilacqua, Davide Bondi



Introduction

- After some very preliminary test presented in LTD11, we fixed a few results on the use of transformers as passive elements for matching TES and conventional electronics.
- Not a new Idea (already used in the past)
- New -> Investigation for a very high noise performance and for a reliable circuital solutions for TES operation.
- Our work has been dedicated specifically to the DC operation with Voltage Bias at low frequency (10KHz).
- AC operation extension are under course (see MAX's talk) and very High-Frequencies seems to open new scenarios.







- Need to work in voltage BIAS-> Z_{TES} > Z_{Lp}
- Current signal is transferred at frequencies < β
- Increase β to cover detector bandwidth (10 KHz)
- Being L_p of typical transformer for low frequencies application at level of tenths of μ H, $Z_{TES} = 0.1-1 \Omega$



Need of integration amplifier like Hi-Fi Amplifier for the pick-up coil signal



- The choice of the transformer is imposed by the noise performance of the amplifier
- We used room temperature amplifiers with 0.6 nV/VHz
- Transf. gain in the range 300-900 (turns ratio)
- High μ core and capability to work in 0.1-4 K range.
- Transformer is on he Mix-Chamber, few cm from TES.





Simulated and measured Transfer Functions







Transf Core selection

Core	F _{max} 300K	F _{max} 77K	θ(77κ)	μ77/μ300	μ4/μ300	Exc noise
Met.glass	>100Кhz	>100Кhz	89.6	76%		yes
**	>100Кhz	>100Кhz	80.8	77%		yes
**	9.6KHz	19Khz	80.0	64%		yes
Mu-metal	31 Hz	282 Hz	80.0	50%		huge
"	20 Hz	58 Hz	80.0	73%		huge
ferrite	>100Кhz	>100Кhz	83.0	8%		yes
"	57Khz	>100Кhz	81.0	6%		yes
"	>100Кhz	51Kz	80.0	84%	82%	yes
spinglass	10.8Khz	9.63kHz	80.0	84%	50%	no
Unknown	>100Кhz	>100Кhz	88.4	99%		small
"	>100Кhz	>100Кhz	86.0	93%		small





Flavio Gatti, TES III, August 17th, 06

10⁵



In a limited region (0.5-5Kz) the current noise equivalent to the input of the transformer is in pA/VHz range.



Flavio Gatti, TES III, August 17 cm, oo



The input noise density given by $R= 1\Omega @ 4KHz$ is measured at different temperatures: it scales as the $T^{1/2}$, as expected.





 Dc bias will require TES working at a proper R value
The Transf. Functions along the transition suggests that AC bias should be preferable (see Geleazzi talk)





Conclusions

- The method of passive cold transformer read-out in trans-resistance configuration is effective (or competitive in term of noise quality) in a limited bandwidth (1 decade: 0.5-5KHz)
- Cold passive electronics, room temperature conventional electronics.
- AC bias configuration should improve the performance, taking the advantage of MUX capability and possibility to extent the bias frequency up to hundreds of MHz.