

Equivalent circuit measurement and complex impedance of calorimeters and bolometers



M. A. Lindeman, K. Barger, D. E. Brandl, S. G. Crowder,
L. Rocks, D. McCammon^{a)}

University of Wisconsin, Madison

Impedance measurements


Impedance of a TES

Z used to understand
Detector physics

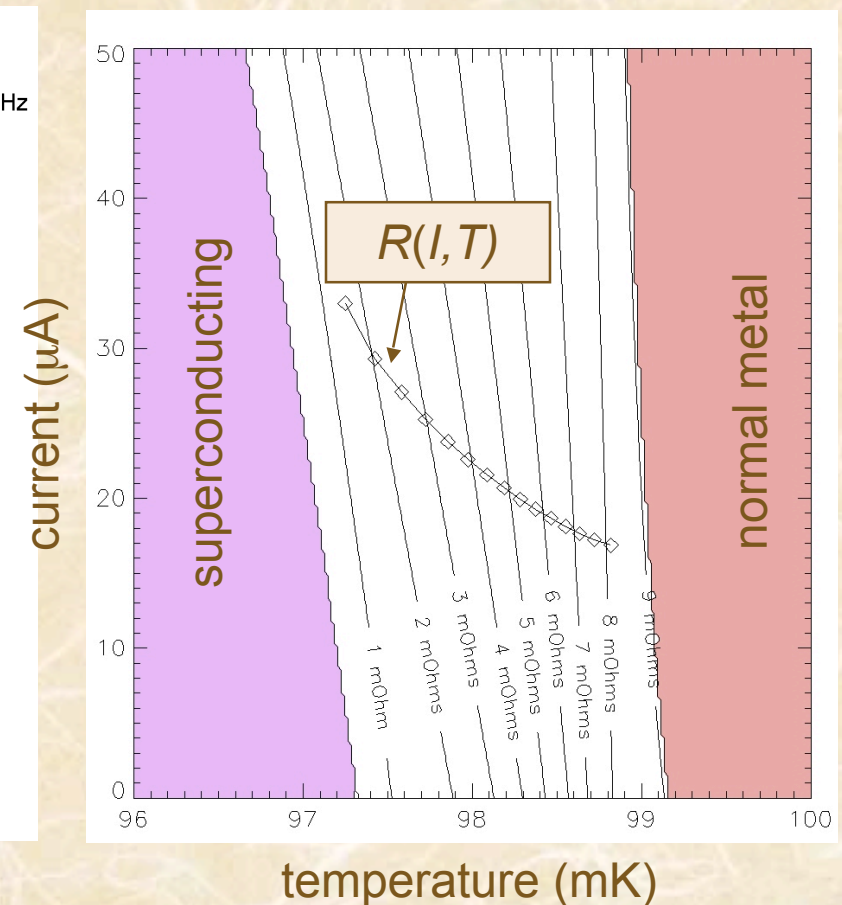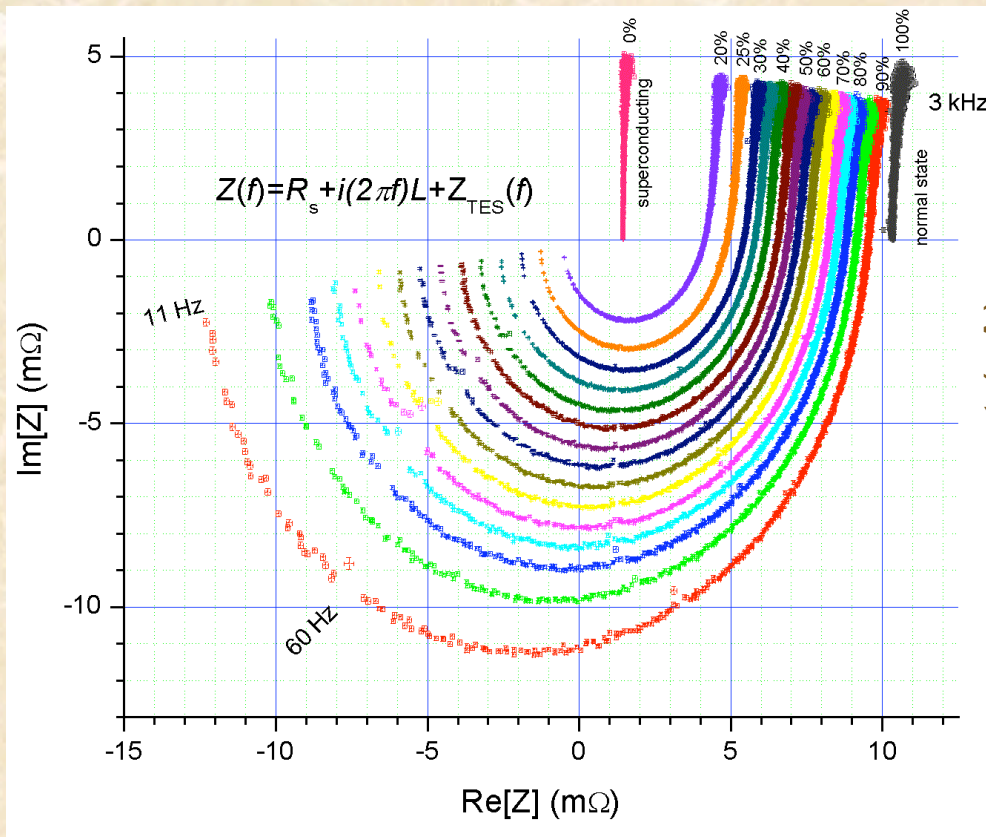


Bias circuit models

Voltage readout
(Si Thermistor)


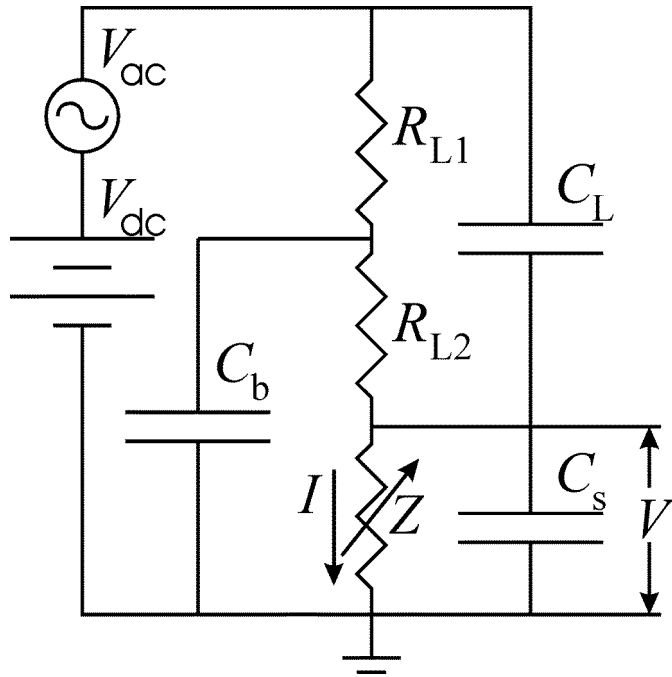


Current Readout
TES

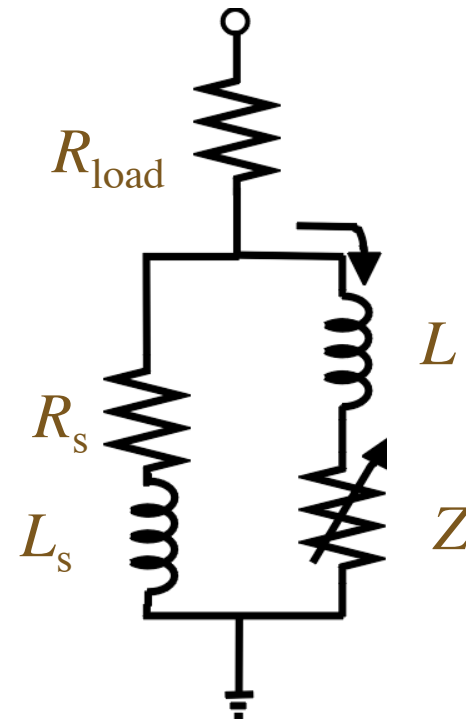




Measurement of transfer functions

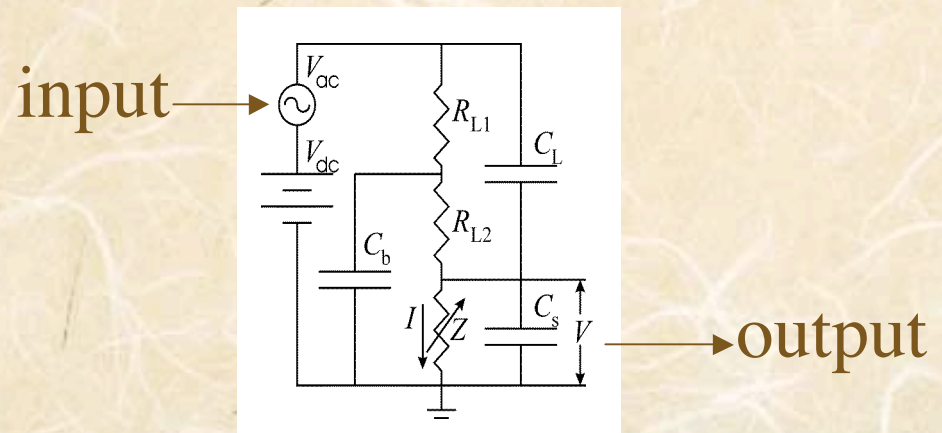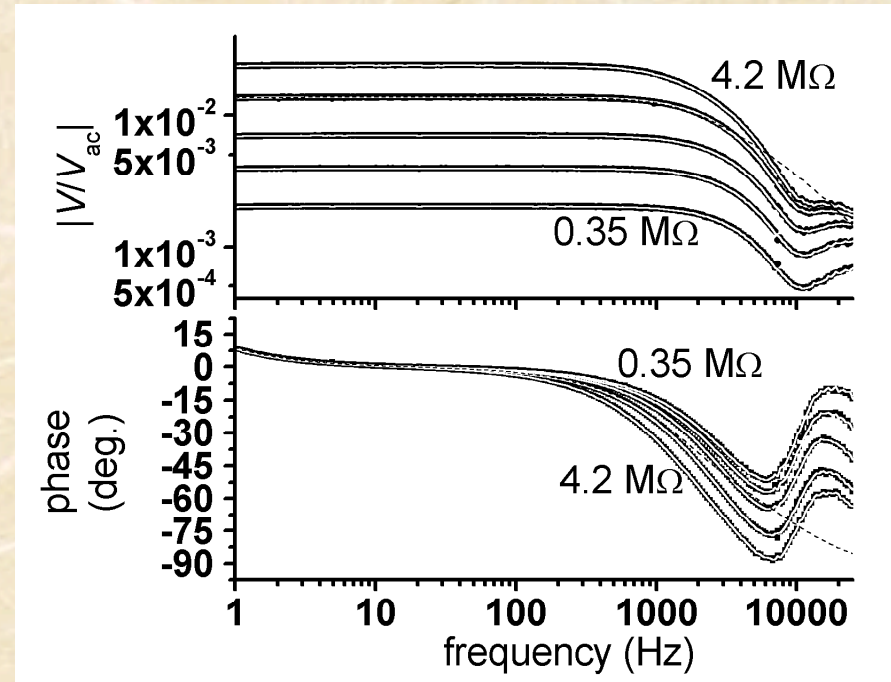- Measure transfer function
 - Put a signal into the bias
 - Measure response at the detector
 - Ratio of output/input is transfer function
- Use with circuit model to calculate $Z(f)$





Non-ideal elements

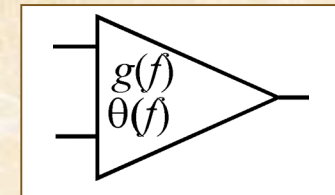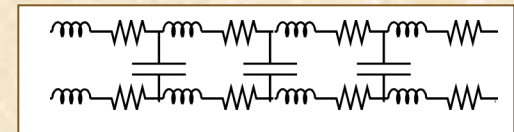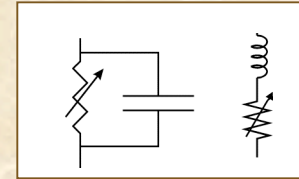- Parasitic impedance
- Distributed loads
- Gain and phase shifts of amplifier are frequency dependent
- All these things affect measurement of $Z(f)$
- May be hard to model every important contribution
- Would like a technique that **easily removes effects of these**




Equivalent circuits

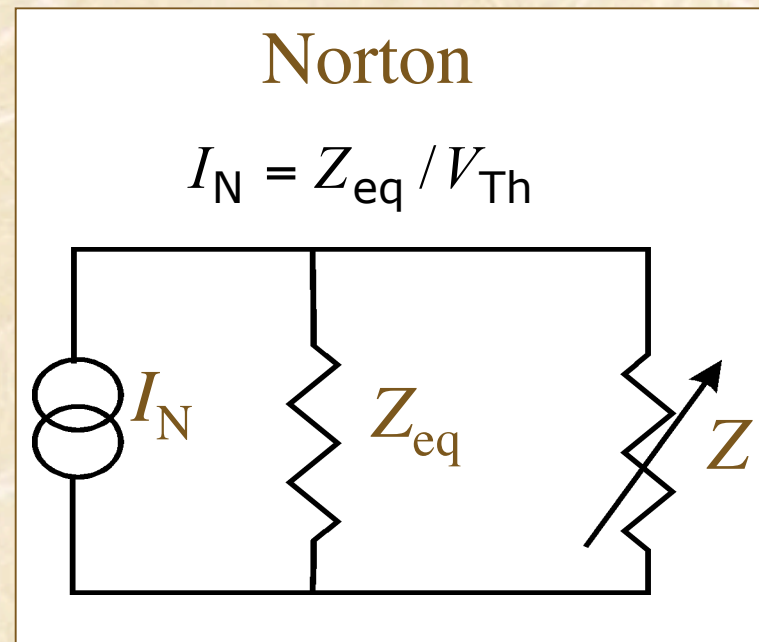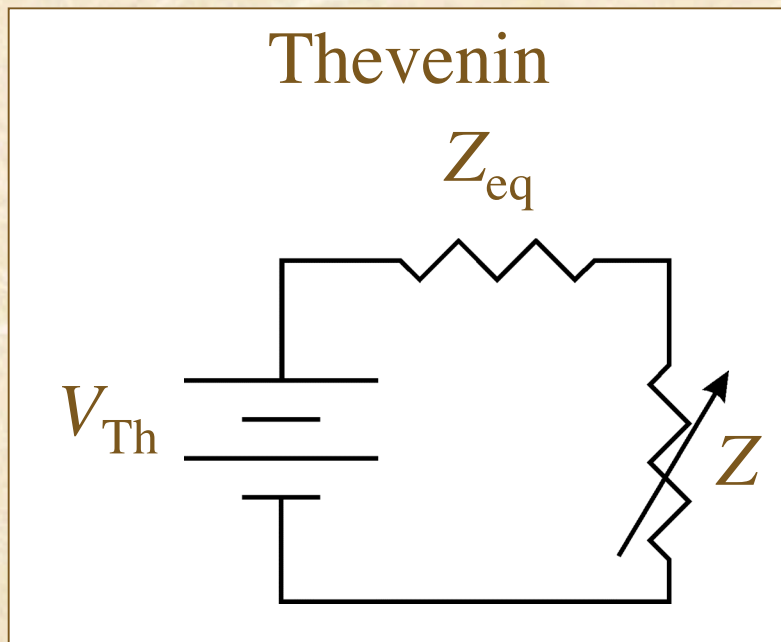- The bias circuit can be replaced by a Thevenin or Norton equivalent circuit
- Equivalents can be measured independently for each frequency
- Allows you to isolate the impedance Z of thermistor



Finding Thevenin / Norton equivalents

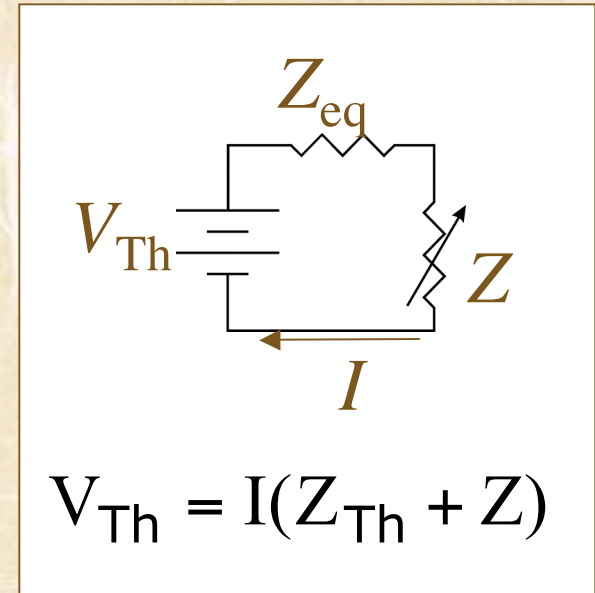- When Z is real valued:
 - Superconducting TES
 - normal metal TES
 - Unbiased Si thermistor or TES
- If Z is real valued resistance R
 - simple relationships between current and resistance




Linear equations:

$$\text{Re}[I^{-1}] = \text{Re}[V_{Th}^{-1}]R + \text{Re}[I_N^{-1}]$$

$$\text{Im}[I^{-1}] = \text{Im}[V_{Th}^{-1}]R + \text{Im}[I_N^{-1}]$$

Linear fits

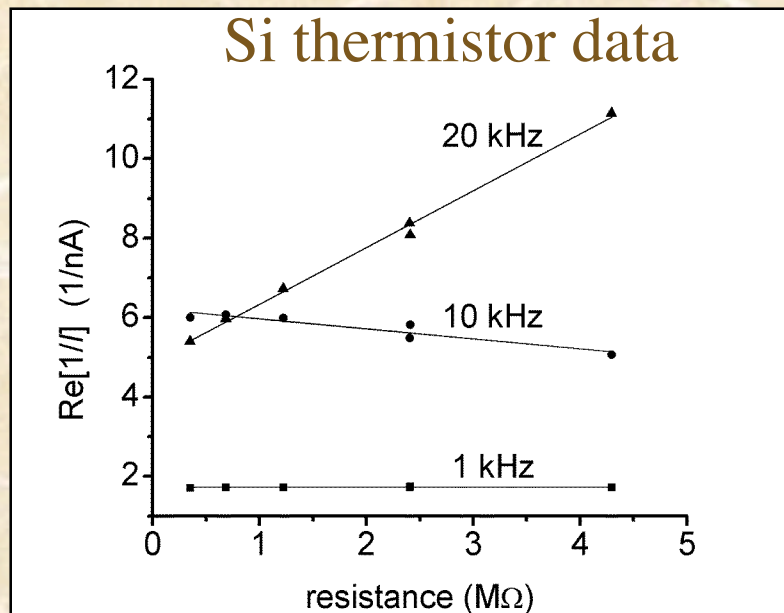
- Choose R of thermistor by setting temperature of the fridge
- $(1/I)$ is a linear function of R
 - Slope gives $(1/V_{Th})$
 - Y-intercept gives $(1/I_N)$
- Find resistance R from low frequency measurements
- Plot $\text{Re}[1/I]$ vs.. R and $\text{Im}[1/I]$ vs.. R
- Results for different frequencies are independent




$$\text{Re}\left[\frac{1}{I}\right] = \left(\frac{1}{V_{Th}}\right)R + \text{Re}\left[\frac{1}{I_N}\right]$$

Measured equivalents

Voltage readout
(Si thermistors)

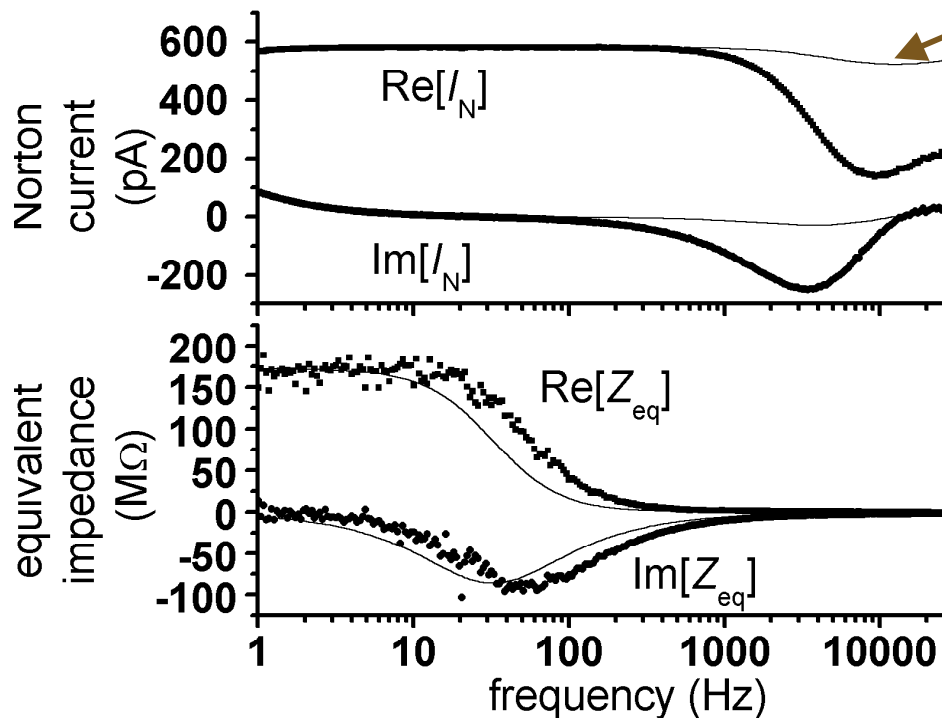


Circuit model not so
Good!

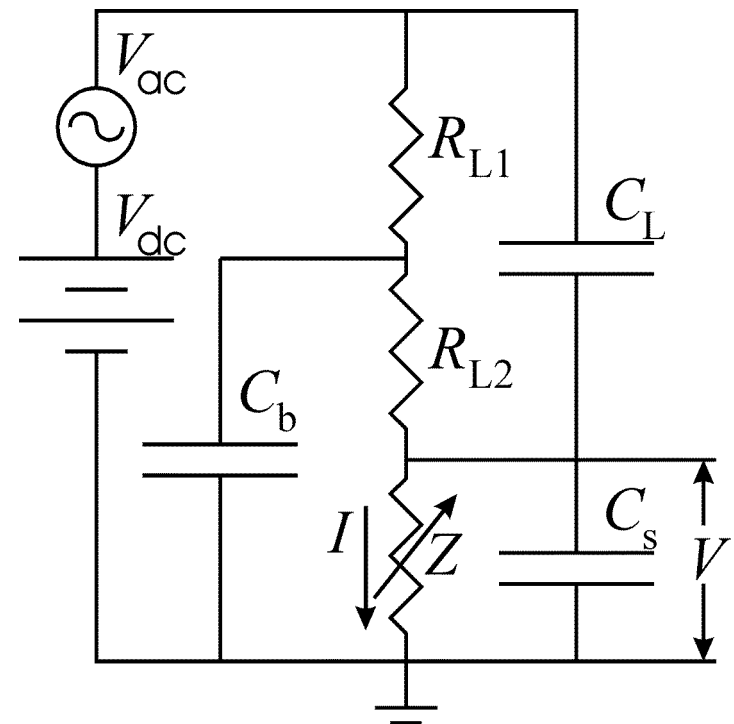

Equivalents of a TES readout

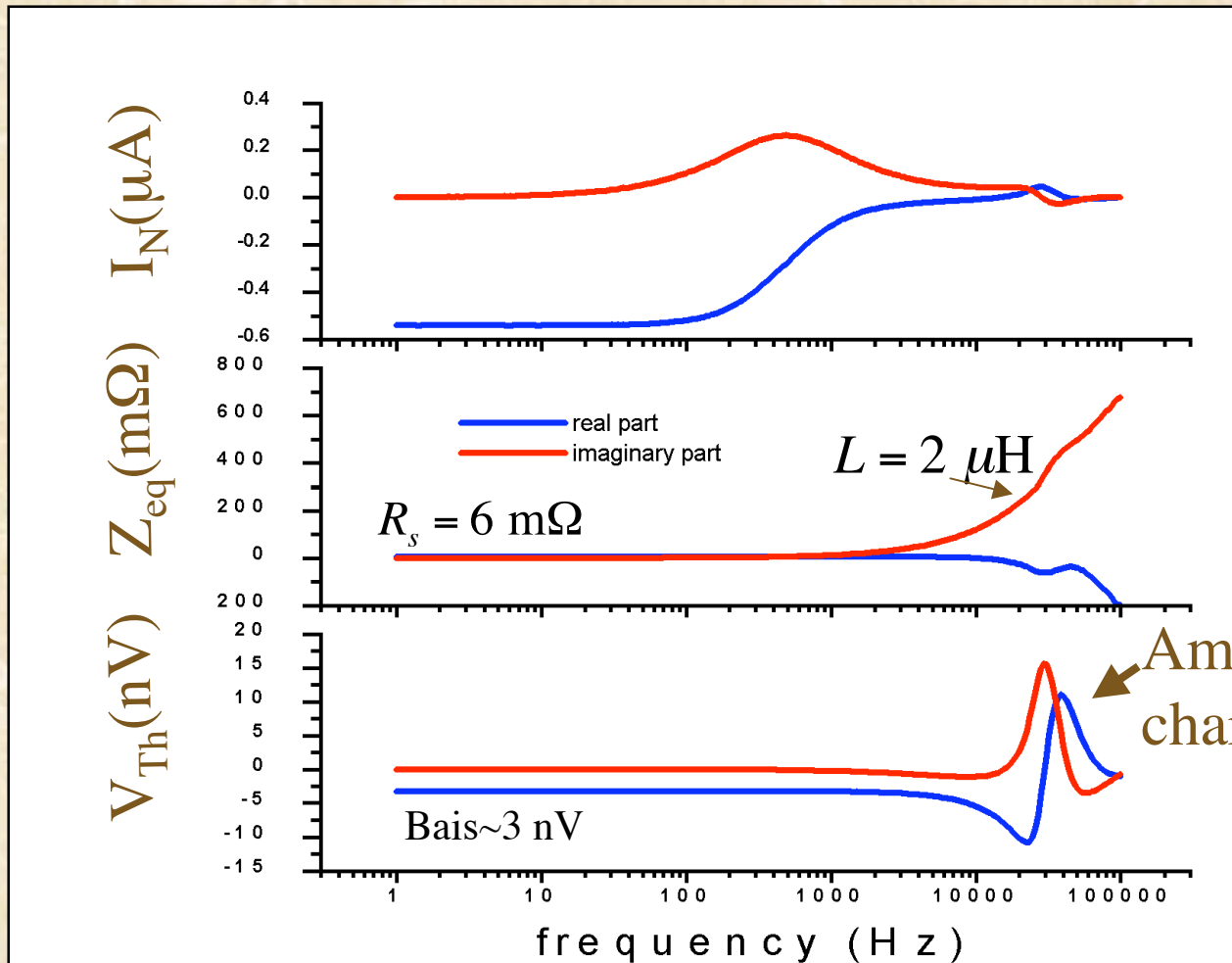Used $R=0$ and $R=R_N$ to find equivalents



Thevenin transform

Voltage readout


$$Z(f) = Z_{\text{eq}}(f) \frac{V(f)}{V_{\text{Th}}(f) - V(f)}$$

or


Current readout

$$Z(f) = Z_{\text{eq}}(f) \left(\frac{I_N(f)}{I(f)} - 1 \right)$$

Transfer function

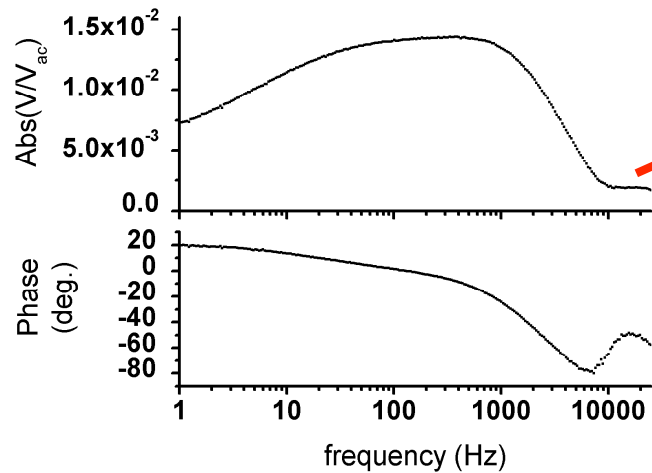


Impedance

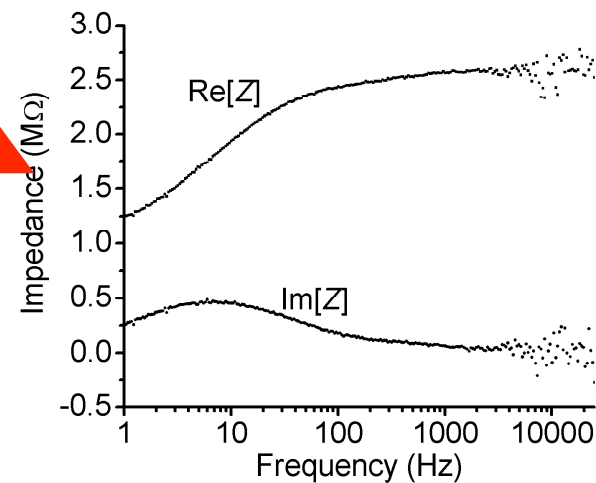


Thevenized Si thermistor data

Impedance vs. Frequency


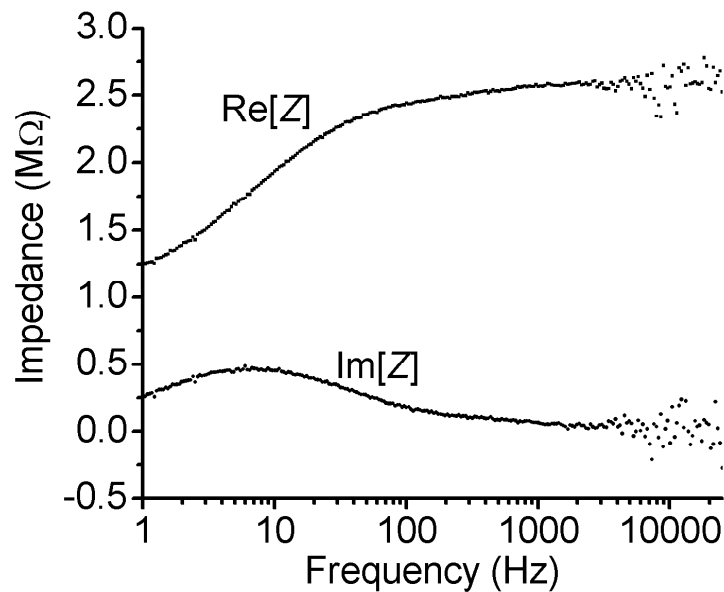


Impedance in the complex plane

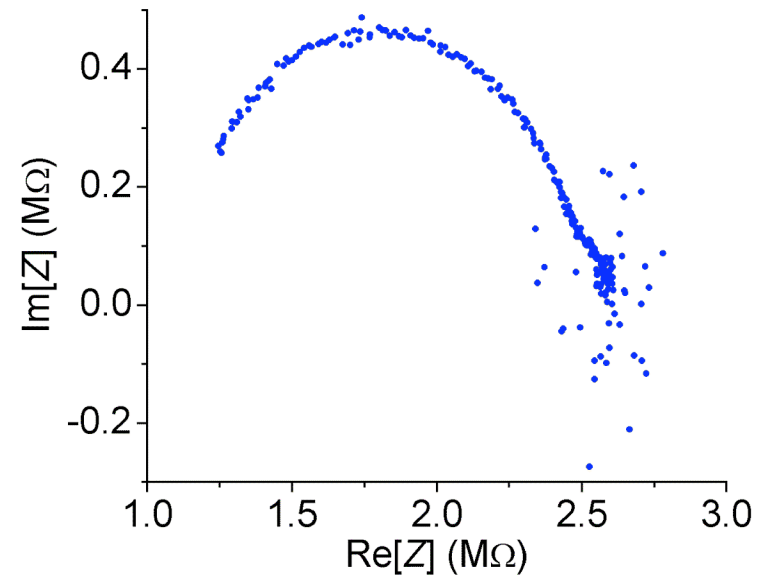


Thevenized TES data

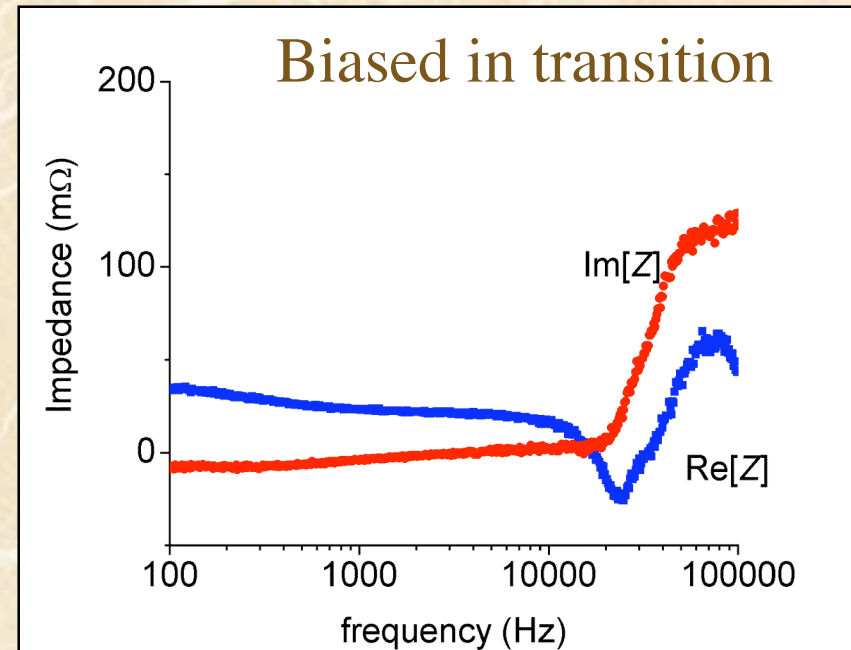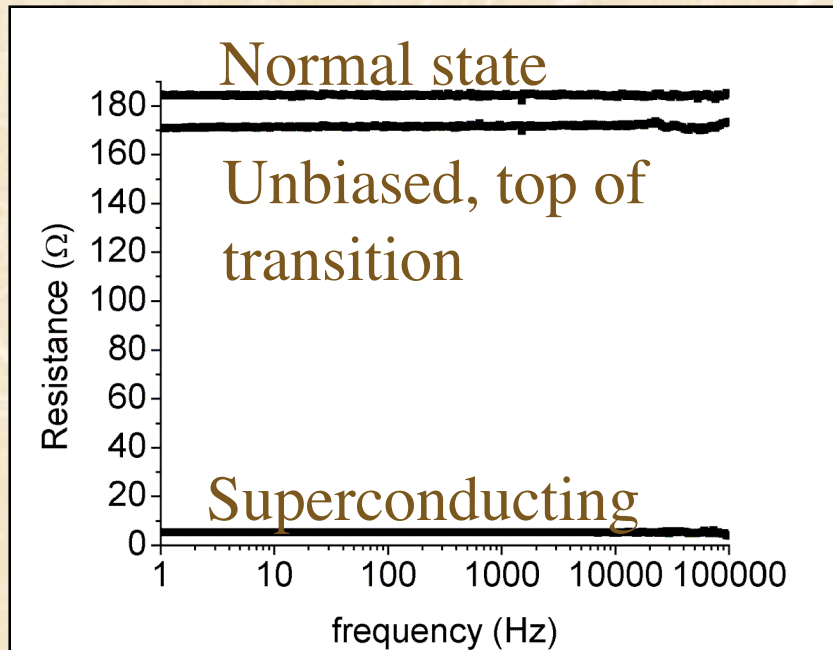- Tested technique on unsuspended TES--very fast time constant
- Real valued measurements worked out as expected
- $Z(f)$ of biased TES in transition--but not as expected



Overview

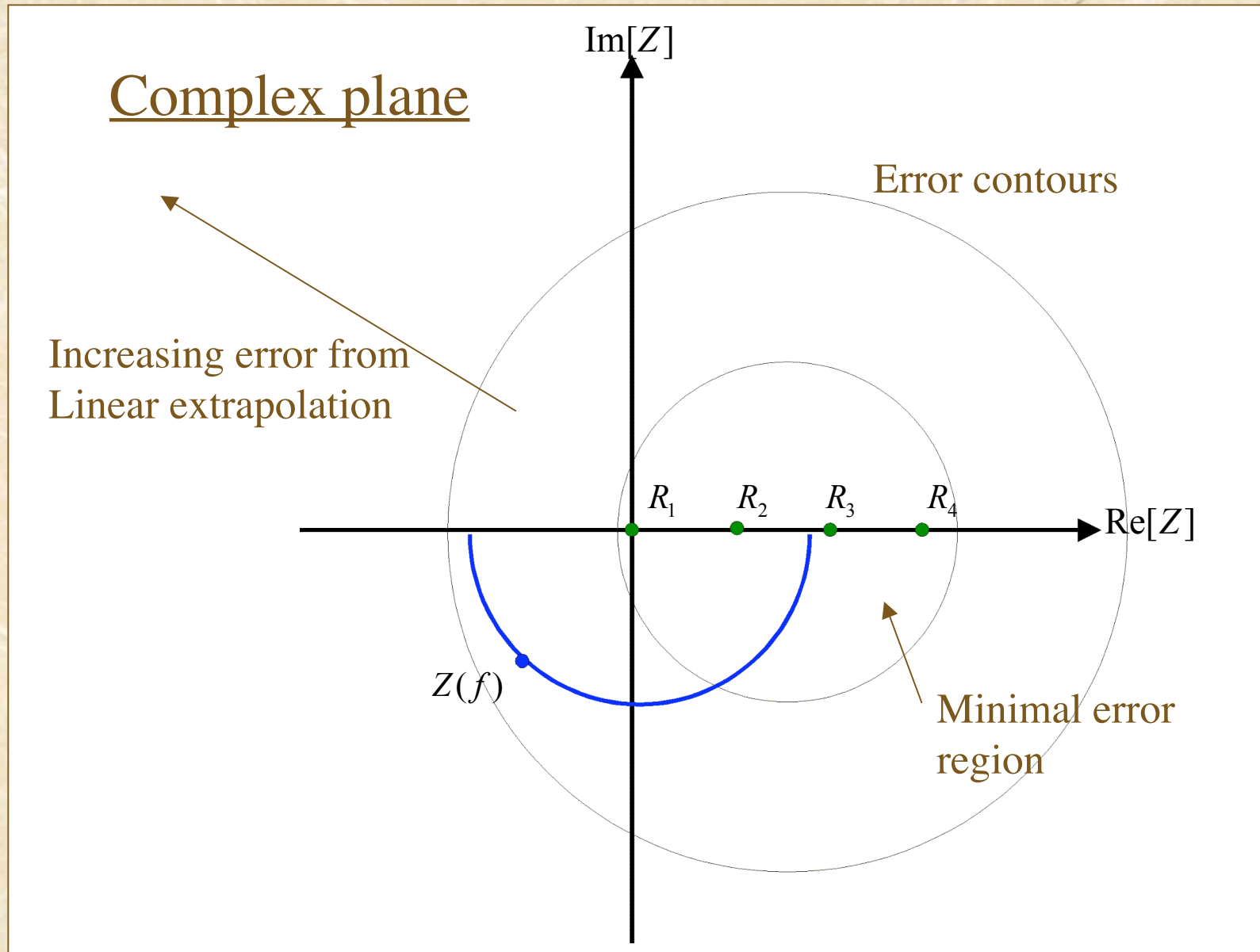

Requirements

- Measure either current or voltage through Z
- Vary the resistance of detector
- Stable gain and phase response from amplifiers
- Measure detector resistance (use low frequency data)

Summary

- Imperfect circuit models introduce **artifacts** in $Z(f)$
- Equivalent circuit method accounts for strays, distributed loads
- Includes gain and phase of amplifiers
- Allows accurate large bandwidth impedance measurements
- Useful for studying physics of calorimeters and bolometers

