

**Chapter 24 Solutions - Problems 1, 3, 4, 7, 11**

1. Figure P24.3 displays a voltage  $v(t)$  versus time  $t$  curve. Its formula is given by Eq. (24.1):

$$v(t) = v_0 \sin(2\pi ft)$$

- a. The maximum voltage can be read off from this curve:

$$V_{\max} = v_0 = \underline{25 \text{ volts}}$$

- b. The rms voltage is  $V_{\max} = \frac{v_0}{\sqrt{2}} = 17.7 \text{ volts}$  (see Sec 24.2)

- c. The period  $T = 1/f$  can be read from the graph:  $T = 0.1 \text{ s}$

- d. The frequency  $f = 1/T = 10 \text{ Hz}$ .

3. The current is described by  $i = 2 \cos(40t) = i_0 \cos(2\pi ft)$

Comparing the last two expressions used immediately we see:

- a. peak current  $i_0 = 2 \text{ A}$

- b. effective current  $I = \frac{i_0}{\sqrt{2}} = 1.41 \text{ A}$

- c. rms current = effective current =  $1.41 \text{ A}$

- d.  $40 = 2\pi f$ , thus  $f \cong 6.37 \text{ Hz}$

4. From the results of Problem 1, we can write:

$$v(t) = 25 \sin(20\pi t)$$

7. The current  $i(t) = 5 \sin(20t)$  flows through a resistor of  $R = 15 \Omega$ . The power lost is given by:

$$P = IV = I^2 R = \left(\frac{25}{2}\right)(15) \text{ W}$$

or  $P = 187.5 \text{ W}$

11. This problem refers to the situation in Fig. 24.5. The capacitance  $C = 2\mu\text{F}$ , the resistance is  $R = 5 \times 10^6 \Omega$ , and the DC voltage of the battery is  $V = 12 \text{ V}$ .

- a. The initial current  $i(0) = V/R = 2.4 \times 10^{-6} \text{ A}$

- b. The time constant  $\tau = RC = 10 \text{ s}$

- c. The final charge  $q(t = \infty) = CV = 2.4 \times 10^{-5} \text{ C}$

- d.  $q(t = RC) = 0.63 CV = 1.51 \times 10^{-5} \text{ C}$

- e.  $i(t = RC) = 0.37 i(0) = 8.9 \times 10^{-7} \text{ A}$