Circuit Diagram (15887)

3-260 MC TUNNEL-DIODE OSCILLATOR

2493486

executive (User)

STD-633 circuit : 3-260 MC TUNNEL-DIODE OSCILLATOR 1 year ago Karma: 1

2009-07-19

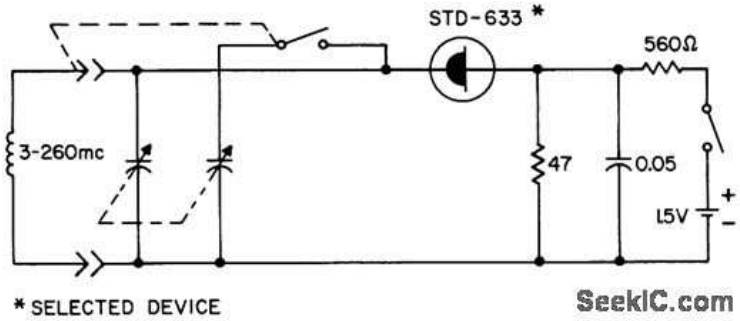

STD-633
Uses plug-in coils to generate sine-wave output over wide frequency range.-"Transistor Manual," Seventh Edition, General Electric Co., 1964, p 352.

© 2009 SeekIC.com Corp.All Rights Reserved.